



Electronics Systems (938II)

Lecture 3.1

Semiconductor Memories – Basic principles

Memories

- They are another fundamental building block that is part of modern electronic systems
 - Processors need memory to work
- Most (if not almost all) memories in modern computers and electronic systems are semiconductor memories
 - They exist(ed) also magnetic and optical memories or storage devices, but they are actually outdated or used only in very few applications

(Semiconductor) Memories - Classification

- Access mode
 - Random Access Memory (RAM)
 - Sequential Access Memory (SAM)
- Supported operation(s)
 - Read-Only Memory (ROM)
 - Read and Write Memory (RWM)

(Semiconductor) Memories - Classification

- Data retention
 - Volatile
 - Non-permanent data
 - Data is lost after the memory is turned off
 - Non-volatile
 - Permanent data
 - Data is retained even when the memory is turned off

Semiconductor Memories - Rationale


- We have already seen an example of semiconductor memory
 - D flip-flop
 - 1x D flip-flop = 1 memory bit
 - It is an example of memory which is volatile and RWM
- D flip-flops are used as memory in computers, but they are expensive in terms of cost, cost per bit, ...
 - There are memories based on semiconductor technologies (such as CMOS) that achieve lower cost per bit or, in other words, higher density per silicon area

Semiconductor Memories - Rationale

- These specialized memory technologies enable a memory cell (1 bit) to be made at a cost of about **1 transistor**

Semiconductor Memories - Rationale

 - These specialized memory technologies enable a memory cell (1 bit) to be made at a cost of about **1 transistor**
 - If you remember, a 1-bit register (or 1 D flip-flop) is made of



Semiconductor Memories - Rationale

- These specialized memory technologies enable a memory cell (1 bit) to be made at a cost of about **1 transistor**
 - If you remember, a 1-bit register (or 1 D flip-flop) is made of
 - 1x NOT gate
 - 2x D latches




Semiconductor Memories - Rationale

- These specialized memory technologies enable a memory cell (1 bit) to be made at a cost of about **1 transistor**

- If you remember, a 1-bit register (or 1 D flip-flop) is made of

 - 1x NOT gate
- 2x D latches
 - Each D latch is made of
 - 4x NAND gates
 - 1x NOT gate




Semiconductor Memories - Rationale

- These specialized memory technologies enable a memory cell (1 bit) to be made at a cost of about **1 transistor**

- If you remember, a 1-bit register (or 1 D flip-flop) is made of

 
- 1x NOT gate
- 2x D latches
 - Each D latch is made of
 - 4x NAND gates
 - 1x NOT gate



Semiconductor Memories - Rationale

- These specialized memory technologies enable a memory cell (1 bit) to be made at a cost of about **1 transistor**

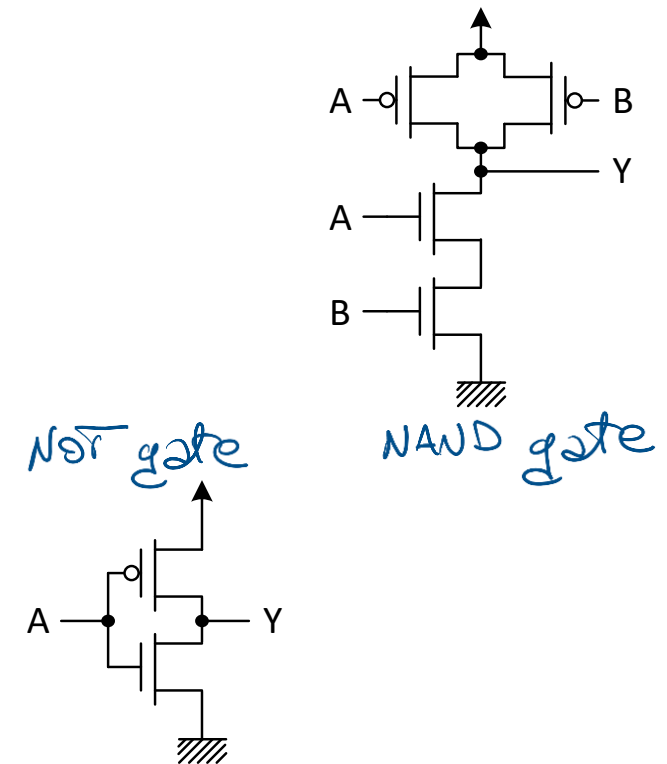
- If you remember, a 1-bit register (or 1 D flip-flop) is made of
 - 1x NOT gate
 - 2x D latches
 - Each D latch is made of
 - 4x NAND gates → 4x (4 transistors) = 16 transistors
 - 1x NOT gate → 1x (2 transistors) = 2 transistors



Semiconductor Memories - Rationale

- These specialized memory technologies enable a memory cell (1 bit) to be made at a cost of about **1 transistor**

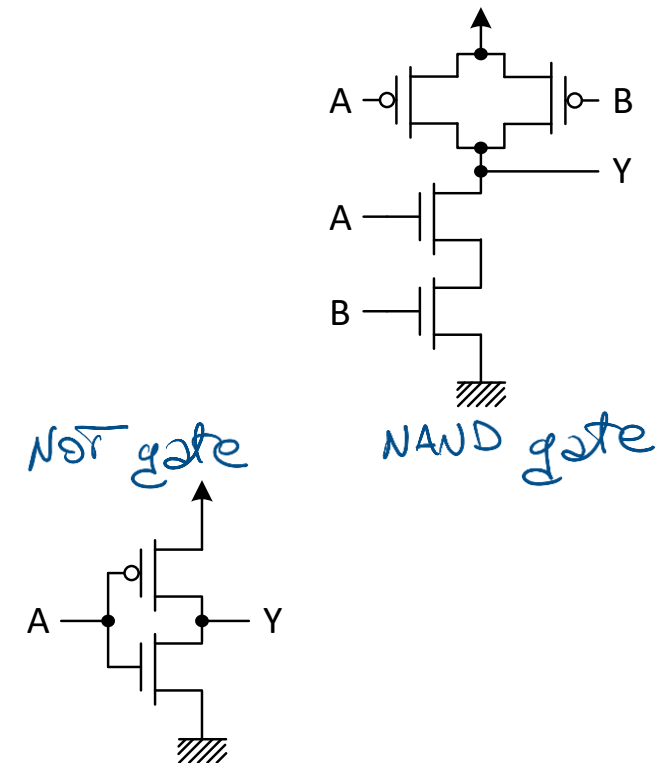
- If you remember, a 1-bit register (or 1 D flip-flop) is made of
 - 1x NOT gate
 - 2x D latches
 - Each D latch is made of \rightarrow 18 transistor
 - 4x NAND gates \rightarrow 4x (4 transistors) = 16 transistors
 - 1x NOT gate \rightarrow 1x (2 transistors) = 2 transistors



Semiconductor Memories - Rationale

- These specialized memory technologies enable a memory cell (1 bit) to be made at a cost of about **1 transistor**

 - If you remember, a 1-bit register (or 1 D flip-flop) is made of
 - 1x NOT gate → 1x (2 transistors) = 2 transistors
 - 2x D latches → 2x (18 transistors) = 36 transistors
 - Each D latch is made of → 18 transistor
 - 4x NAND gates → 4x (4 transistors) = 16 transistors
 - 1x NOT gate → 1x (2 transistors) = 2 transistors



Semiconductor Memories - Rationale

- These specialized memory technologies enable a memory cell (1 bit) to be made at a cost of about **1 transistor**
- If you remember, a 1-bit register (or 1 D flip-flop) is made of **38 transistors**!
 - 1x NOT gate → 1x (2 transistors) = 2 transistors
 - 2x D latches → 2x (18 transistors) = 36 transistors
 - Each D latch is made of → 18 transistor
 - 4x NAND gates → 4x (4 transistors) = 16 transistors
 - 1x NOT gate → 1x (2 transistors) = 2 transistors

Semiconductor Memories - Rationale

- These specialized memory technologies enable a memory cell (1 bit) to be made at a cost of about **1 transistor**
 - If you remember, a 1-bit register (or 1 D flip-flop) is made of **38 transistors!**
- This was an academic example
 - A real-world CMOS D flip-flop consists of fewer transistors
 - However, looking at a real-world CMOS technology (7 nm) ...

Semiconductor Memories - Rationale

- These specialized memory technologies enable a memory cell (1 bit) to be made at a cost of about **1 transistor**
 - If you remember, a 1-bit register (or 1 D flip-flop) is made of **38 transistors!**
- This was an academic example
 - A real-world CMOS D flip-flop consists of fewer transistors
 - However, looking at a real-world CMOS technology (7 nm) ...
 - Area of a NAND gate $\cong 0.0768 \mu^2$

Semiconductor Memories - Rationale

- These specialized memory technologies enable a memory cell (1 bit) to be made at a cost of about **1 transistor**
 - If you remember, a 1-bit register (or 1 D flip-flop) is made of **38 transistors!**
- This was an academic example
 - A real-world CMOS D flip-flop consists of fewer transistors
 - However, looking at a real-world CMOS technology (7 nm) ...
 - Area of a NAND gate $\cong 0.0768 \mu^2 \rightarrow$ area of 1 transistor $\cong \frac{0.0768}{4} \mu^2 = 0.0192 \mu^2$

Semiconductor Memories - Rationale

- These specialized memory technologies enable a memory cell (1 bit) to be made at a cost of about **1 transistor**
 - If you remember, a 1-bit register (or 1 D flip-flop) is made of **38 transistors**!
- This was an academic example
 - A real-world CMOS D flip-flop consists of fewer transistors
 - However, looking at a real-world CMOS technology (7 nm) ...
 - Area of a NAND gate $\cong 0.0768 \mu^2 \rightarrow$ area of 1 transistor $\cong \frac{0.0768}{4} \mu^2 = 0.0192 \mu^2$
 - Area of a DFF $\cong 0.4032 \mu^2$

Semiconductor Memories - Rationale

- These specialized memory technologies enable a memory cell (1 bit) to be made at a cost of about **1 transistor**
 - If you remember, a 1-bit register (or 1 D flip-flop) is made of **38 transistors**!
- This was an academic example
 - A real-world CMOS D flip-flop consists of fewer transistors
 - However, looking at a real-world CMOS technology (7 nm) ...
 - Area of a NAND gate $\cong 0.0768 \mu^2 \rightarrow$ area of 1 transistor $\cong \frac{0.0768}{4} \mu^2 = 0.0192 \mu^2$
 - Area of a DFF $\cong 0.4032 \mu^2 \rightarrow \frac{0.4032}{0.0192} = 21$

Semiconductor Memories - Rationale

- These specialized memory technologies enable a memory cell (1 bit) to be made at a cost of about **1 transistor**
 - If you remember, a 1-bit register (or 1 D flip-flop) is made of **38 transistors**!
- This was an academic example
 - A real-world CMOS D flip-flop consists of fewer transistors
 - However, looking at a real-world CMOS technology (7 nm) ...
 - Area of a NAND gate $\cong 0.0768 \mu^2 \rightarrow$ area of 1 transistor $\cong \frac{0.0768}{4} \mu^2 = 0.0192 \mu^2$
 - Area of a DFF $\cong 0.4032 \mu^2 \rightarrow \frac{0.4032}{0.0192} = 21 \rightarrow$ **One DFF is about 21 transistors**

Semiconductor Memories - Rationale

- We are going to see different types of semiconductor memories
 - All the main ones used in modern electronic systems

Semiconductor Memories - Rationale

- We are going to see different types of semiconductor memories
 - All the main ones used in modern electronic systems
- But first, let's take a look at the outline of the architecture of semiconductor memories
 - It is common to all of them (Read only / RW ... it's the same)

Semiconductor Memories – Architecture outline


- The architecture of semiconductor memories has a **matrix** shape
 - Two dimensions
 - **Bi-dimensional addressing**

Semiconductor Memories – Architecture outline

- The architecture of semiconductor memories has a **matrix** shape
 - Two dimensions
 - **Bi-dimensional addressing**
- **Why not a vector shape?** *Lowh costs mainly*
 - For two main reason

Semiconductor Memories – Architecture outline

 1. **Compatibility with manufacturing process** *Manufacturing process*
 - Semiconductor systems/devices are fabricated by processing a circular die of silicon (typically called wafer)




Wafer shape

Semiconductor Memories – Architecture outline

 1. Compatibility with manufacturing process

- Semiconductor systems/devices are fabricated by processing a circular die of silicon (typically called wafer)
- Using a **matrix shape**, some parts of the wafer are wasted



Wafer shape

Semiconductor Memories – Architecture outline

1. Compatibility with manufacturing process

- Semiconductor systems/devices are fabricated by processing a circular die of silicon (typically called wafer)
- If a **vector shape** is used, more parts of the wafer are wasted



Wafer shape

Semiconductor Memories – Architecture outline

2. Resource cost *Monodimensional addressing!*
- Suppose that L bits of address are required
 - Vector shape
 - Mono-dimensional addressing $\rightarrow 2^L$ addresses
 - Matrix shape
 - Bi-dimensional addressing
 - Assuming to split L as $L = N + M$
 - 2^N addresses for one dimension
 - 2^M addresses for the other dimension
 - Total: $2^N + 2^M$ addresses *Less addresses.*

Semiconductor Memories – Architecture outline

2. Resource cost

- Suppose that L bits of address are required
 - Vector shape
 - Resource cost = logic resources to decode 2^L addresses
 - Matrix shape
 - Resource cost = logic resources to decode $2^N + 2^M$ addresses
 - With $L = N + M \rightarrow 2^L = 2^{N+M} = 2^N \cdot 2^M$
 - $2^N \cdot 2^M > 2^N + 2^M$???

Semiconductor Memories – Architecture outline

2. Resource cost


- Suppose that L bits of address are required: $L = N + M$
 - $2^N \cdot 2^M > 2^N + 2^M$

Semiconductor Memories – Architecture outline

2. Resource cost

- Suppose that L bits of address are required: $L = N + M$

- $2^N \cdot 2^M > 2^N + 2^M$

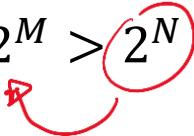

Semiconductor Memories – Architecture outline

2. Resource cost

- Suppose that L bits of address are required: $L = N + M$
 - $2^N \cdot 2^M > 2^N + 2^M$
 - $2^N \cdot (2^M - 1) > 2^M$

Semiconductor Memories – Architecture outline

2. Resource cost

- Suppose that L bits of address are required: $L = N + M$

- $2^N \cdot 2^M > 2^N + 2^M$

- $2^N \cdot (2^M - 1) > 2^M$

Semiconductor Memories – Architecture outline

2. Resource cost

- Suppose that L bits of address are required: $L = N + M$

- $2^N \cdot 2^M > 2^N + 2^M$

- $2^N \cdot (2^M - 1) > 2^M$

- $2^N > \frac{2^M}{(2^M - 1)}$

Semiconductor Memories – Architecture outline

2. Resource cost

- Suppose that L bits of address are required: $L = N + M$

- $2^N > \frac{2^M}{(2^M - 1)}$

- Some numeric examples

– $N = M = 1$	$\rightarrow 2 > \frac{2}{2-1}$	$\rightarrow 2 > \frac{2}{1}$	$\rightarrow 2 = 2$	(NO)
– $N = 1, M = 2$	$\rightarrow 2 > \frac{4}{4-1}$	$\rightarrow 2 > \frac{4}{3}$	$\rightarrow 2 > 1.3333$	(YES) ✓
– $N = 2, M = 1$	$\rightarrow 4 > \frac{2}{2-1}$	$\rightarrow 4 > \frac{2}{1}$	$\rightarrow 4 > 2$	(YES)
– $N = 3, M = 7$	$\rightarrow 8 > \frac{128}{128-1}$	$\rightarrow 8 > \frac{128}{127}$	$\rightarrow 8 > 1.008$	(YES)
– ...				

Non realistic examples

In theory not always satisfied, in reality it is always.

Semiconductor Memories – Architecture outline

2. Resource cost

- Suppose that L bits of address are required: $L = N + M$

- $2^N > \frac{2^M}{(2^M - 1)}$

- A more realistic example:

- 1 Mbit of memory $\cong 2^{20} \rightarrow L = 20$

- Assume $N = 8$ and $M = 12$

- $256 > \frac{4096}{4096-1} \rightarrow 256 > \frac{4096}{4095} \rightarrow 256 \gg \sim 1$

Cost to decode addresses is much higher
if we don't, you would need more
subcarriers

Semiconductor Memories – Architecture outline

2. Resource cost

- Suppose that L bits of address are required: $L = N + M$
 - $2^N > \frac{2^M}{(2^M - 1)}$
 - A more realistic example:
 - 1 Mbit of memory $\cong 2^{20} \rightarrow L = 20$
 - Assume $N = 8$ and $M = 12$
 - $256 > \frac{4096}{4096 - 1} \rightarrow 256 > \frac{4096}{4095} \rightarrow 256 \gg \sim 1$
 - In other words, assuming realistic examples, it happens that $2^L \gg 2^N + 2^M$!!!


Semiconductor Memories – Architecture outline

2. Resource cost

- Suppose that L bits of address are required: $L = N + M$
 - $2^N > \frac{2^M}{(2^M - 1)}$
 - A more realistic example:
 - 1 Mbit of memory $\cong 2^{20} \rightarrow L = 20$
 - Assume $N = 8$ and $M = 12$
 - $256 > \frac{4096}{4096 - 1} \rightarrow 256 > \frac{4096}{4095} \rightarrow 256 \gg \sim 1$
 - In other words, assuming realistic examples, it happens that $2^L \gg 2^N + 2^M$!!!
 - **Bi-dimensional addressing requires far fewer resources for address decoding !!!**

Semiconductor Memories – Architecture outline


- Draft

 

Semiconductor Memories – Architecture outline

- Draft

- WL_i = Word Line

 


Semiconductor Memories – Architecture outline

- Draft

- WL_i = Word Line

- BL_j = Bit Line

 

Semiconductor Memories – Architecture outline

- Draft


- WL_i = Word Line

- BL_j = Bit Line

- Memory cell

- Typically contains 1 transistor
 - Or something different, but with “similar” cost in terms of silicon area

 each cell is linked to just one WL and BL




Semiconductor Memories – Architecture outline

- Draft
 - To complete the architecture, they are required
 - A row decoder (or x-decoder)
 - For decoding the Word Line address
 - A column decoder (or y-decoder)
 - For decoding the Bit Line address


Semiconductor Memories – Architecture outline

- Final

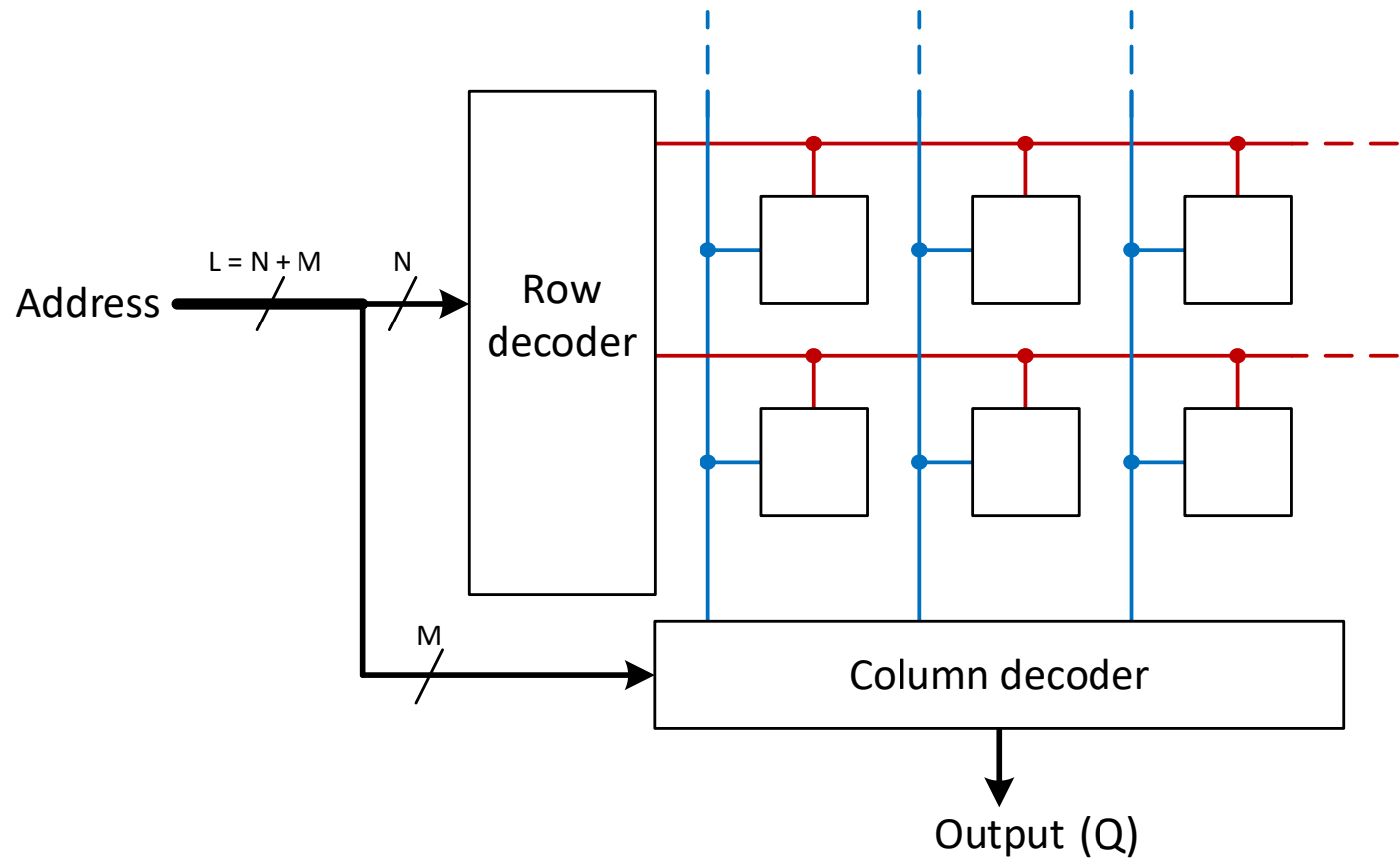

Semiconductor Memories – Architecture outline

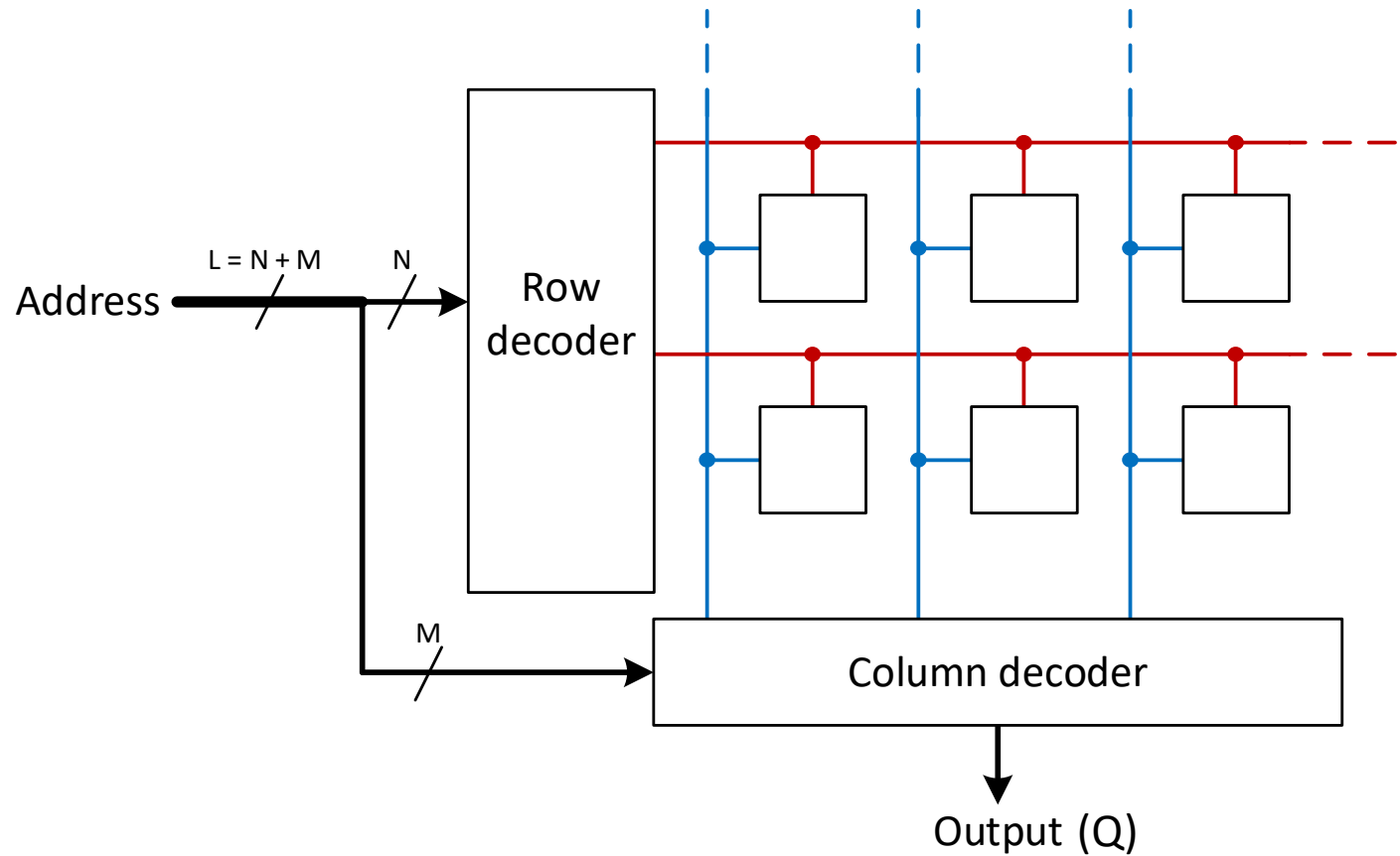
- Final – Read-Only Memory
 - But only for ROM
 - Just output (Q)



Semiconductor Memories – Architecture outline

- Final – Read-Only Memory
 - But only for ROM
 - Just output (Q)
- In case of RWM, an I/O block is required
 - And a Read/Write (R/W) signal


1 bit memory cells! So 1 bit output!

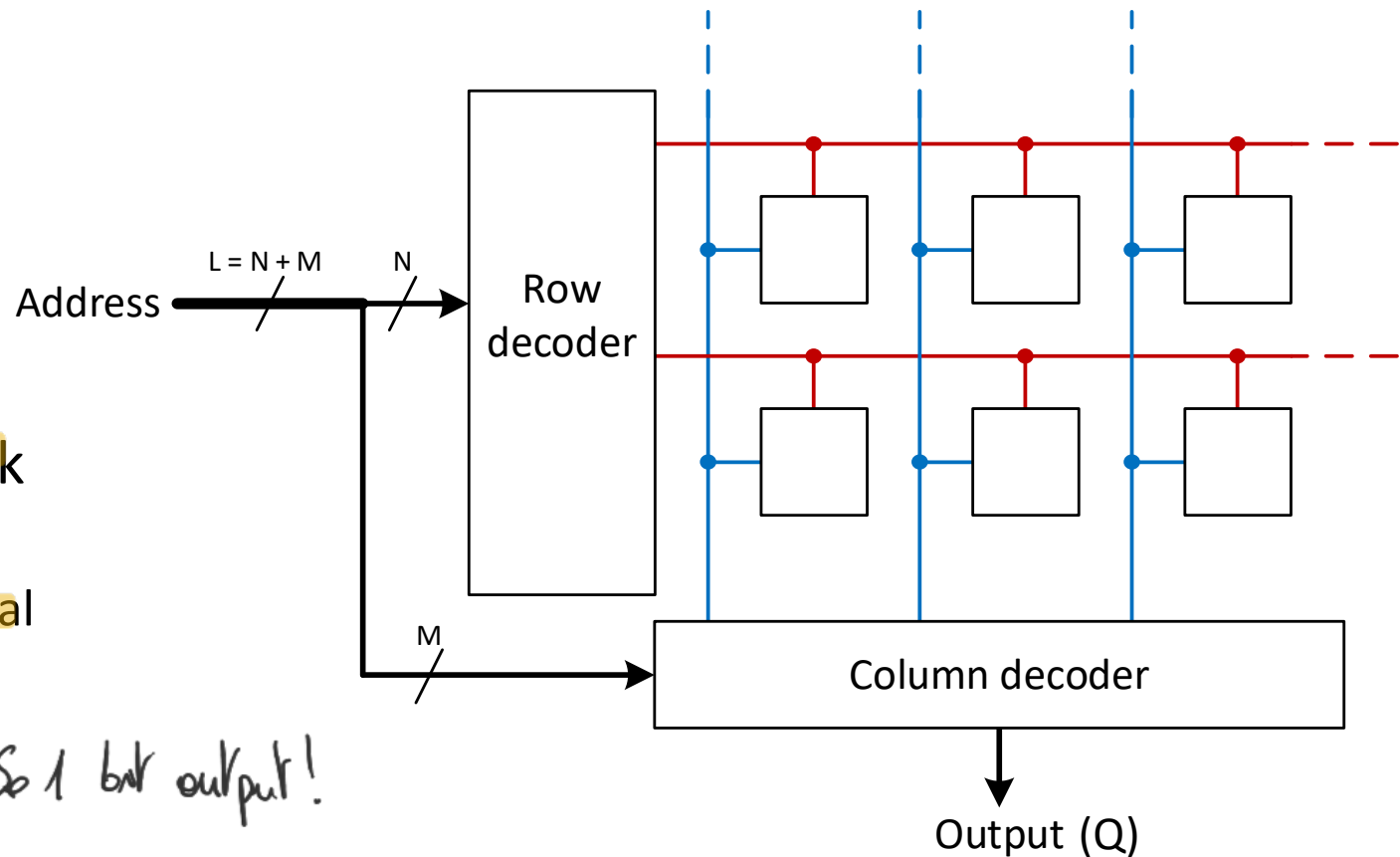

Semiconductor Memories – Architecture outline

- Final – Read-Write Memory (RWM)

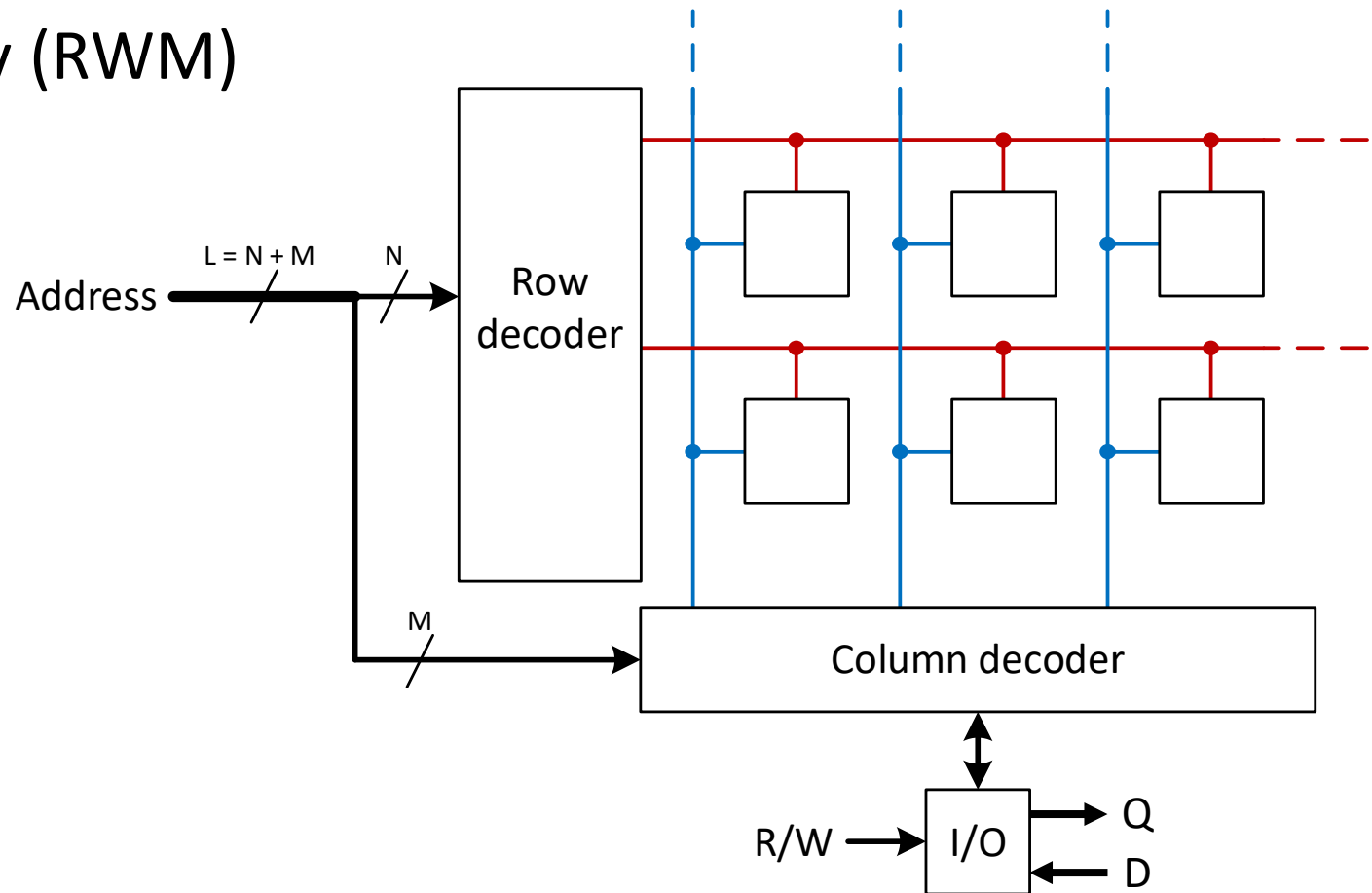- D = input data (bit) *16bit*
- Q = output data (bit) *16bit*



Semiconductor Memories – Architecture outline

- The architecture shown before is the one for single-bit memories
 - Each memory cell store 1 bit
 - Read or Write of 1 bit at a time
- Multi-bit memories are built by connecting in parallel single-bit memories
 - Assuming
 - Number of memory cells = $2^L \rightarrow L = N + M$ bits of address
 - Bit length = b (bits)
 - Memory is organized as $2^L \times b$
 - Data (of b bits) is called word


Semiconductor Memories – Architecture outline

- Multi-bit memory: $2^L \times b$
 - b parallel single-bit block
 - Each single bit block
 - Contains 2^L (single-bit) memory cells
 - That are arranged as a matrix of from $2^N \cdot 2^M$
 - Typically, L is an integer multiple of 10, so that ...
 - $L = 10 \rightarrow 2^{10} \rightarrow k$ (kilo)
 - $L = 20 \rightarrow 2^{20} \rightarrow M$ (Mega)
 - $L = 30 \rightarrow 2^{30} \rightarrow G$ (Giga)

Semiconductor Memories – Architecture outline

- Multi-bit memory: $2^L \times b$
 - Example of a 32k x 8 memory
 - $32k = 2^5 * 2^{10} = 2^{15} \rightarrow$ 15 bits for address
 - $b = 8 \rightarrow$ 8 parallel single-bit-output memory blocks

Logically in parallel

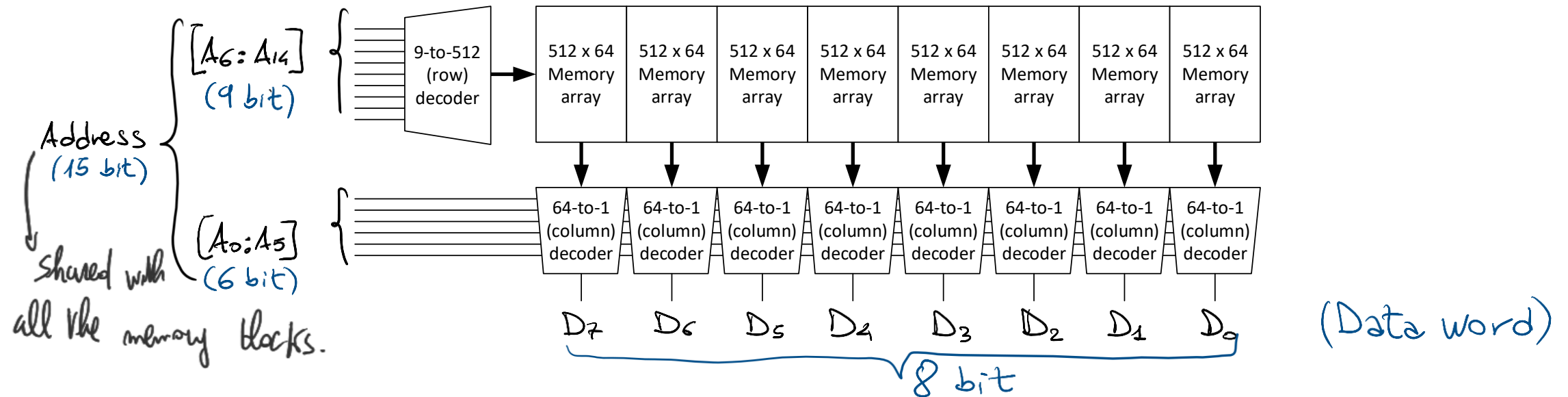



Thank you for your attention

Luca Crocetti
(luca.crocetti@unipi.it)