



# Electronics Systems (938II)

Lecture 2.4

Building Blocks of Electronic Systems – Finite State Machine

# Finite State Machine (FSM)

- A **Finite State Machine (FSM)** is a **sequential circuit** that:
  - Has a finite (limited) **number of states**
  - Is in **exactly one of the finite states at any given time**
- The **evolution** between the states **depends** on
  - **Inputs**
  - **Current state**
  - In fact, it is a sequential circuit


# Finite State Machine (FSM)

- Memory resources are required to store the current state
  - We have already seen an example
    - Latches
    - Flip-flops/Registers
  - If the FSM employs latches, it is asynchronous
  - If it employs a register, it is synchronous
    - By default, we will assume synchronous FSM in the next slides
    - This means that the state change occurs on the rising edge of the clock signal

Sep. networks: our ws  
assigned only on  
the edge of the clock  
if we have synchronous  
machines.


# Finite State Machine (FSM)

- Outline of an FSM

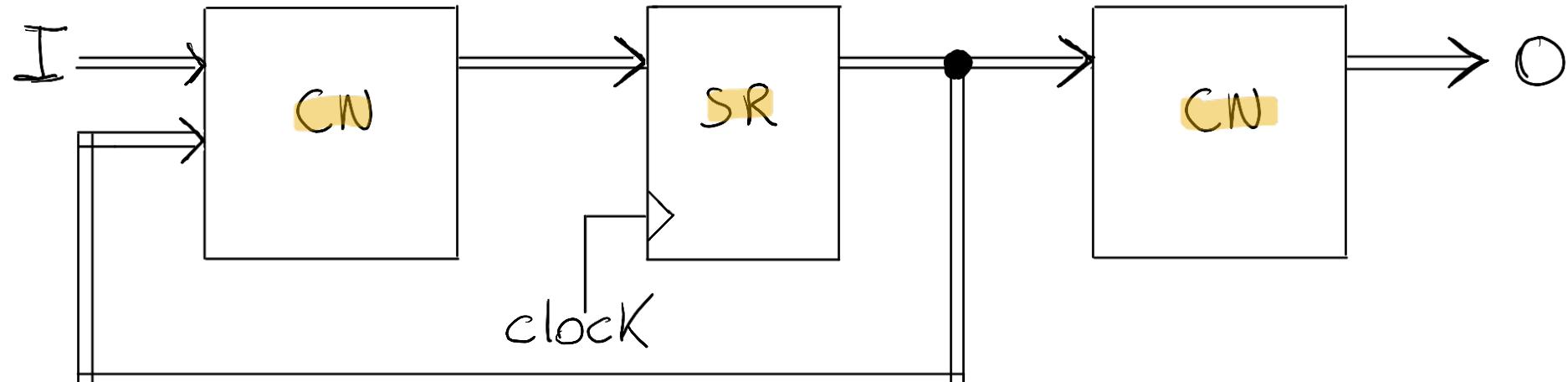


# Finite State Machine (FSM)

- Outline of an FSM

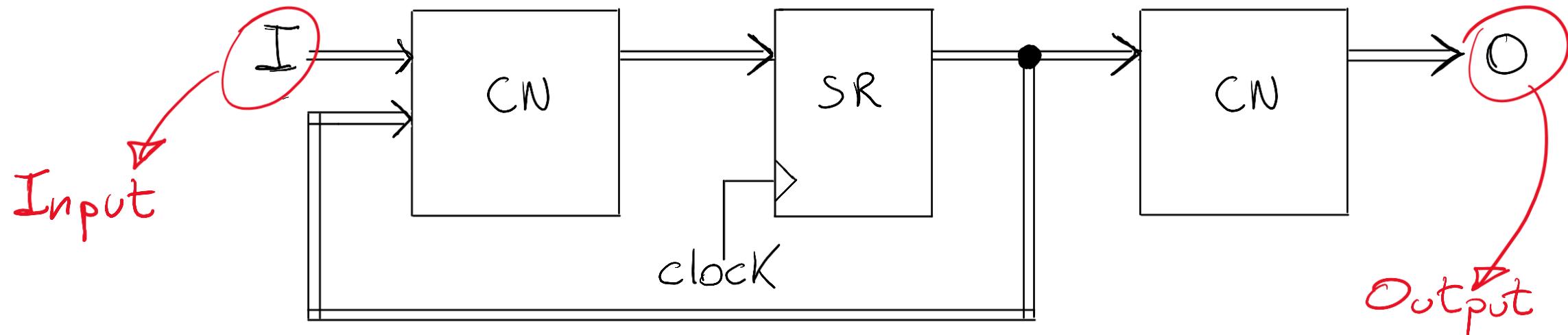


# Finite State Machine (FSM)

- Outline of an FSM

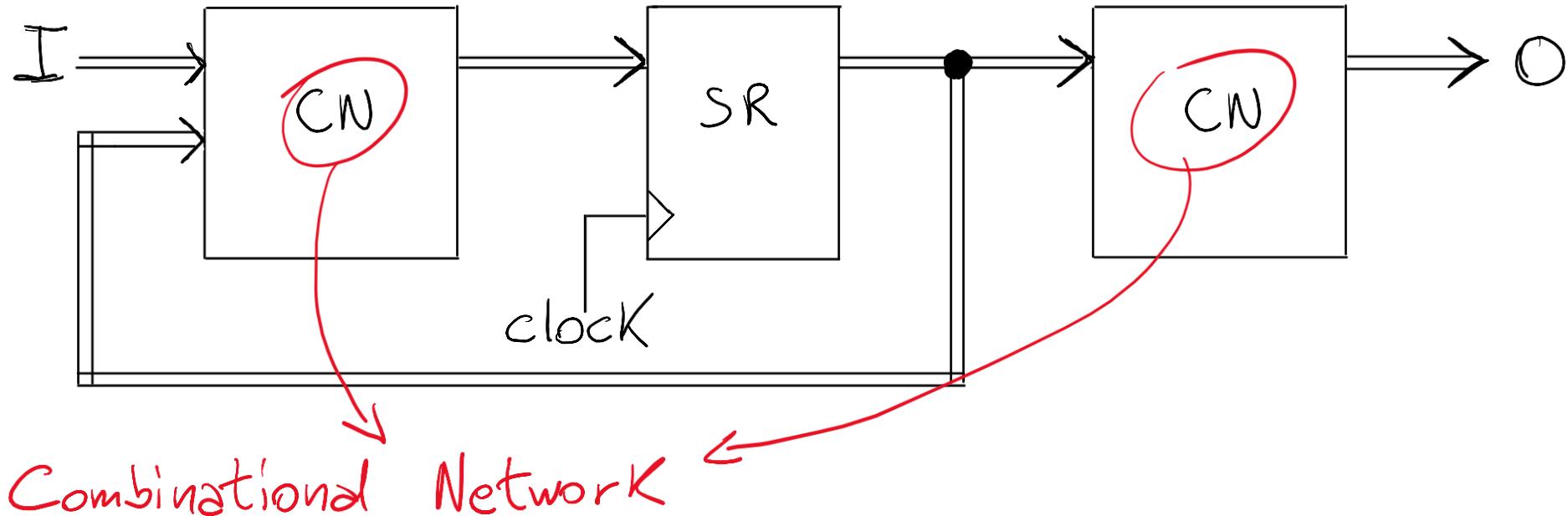


# Finite State Machine (FSM)

- Outline of an FSM

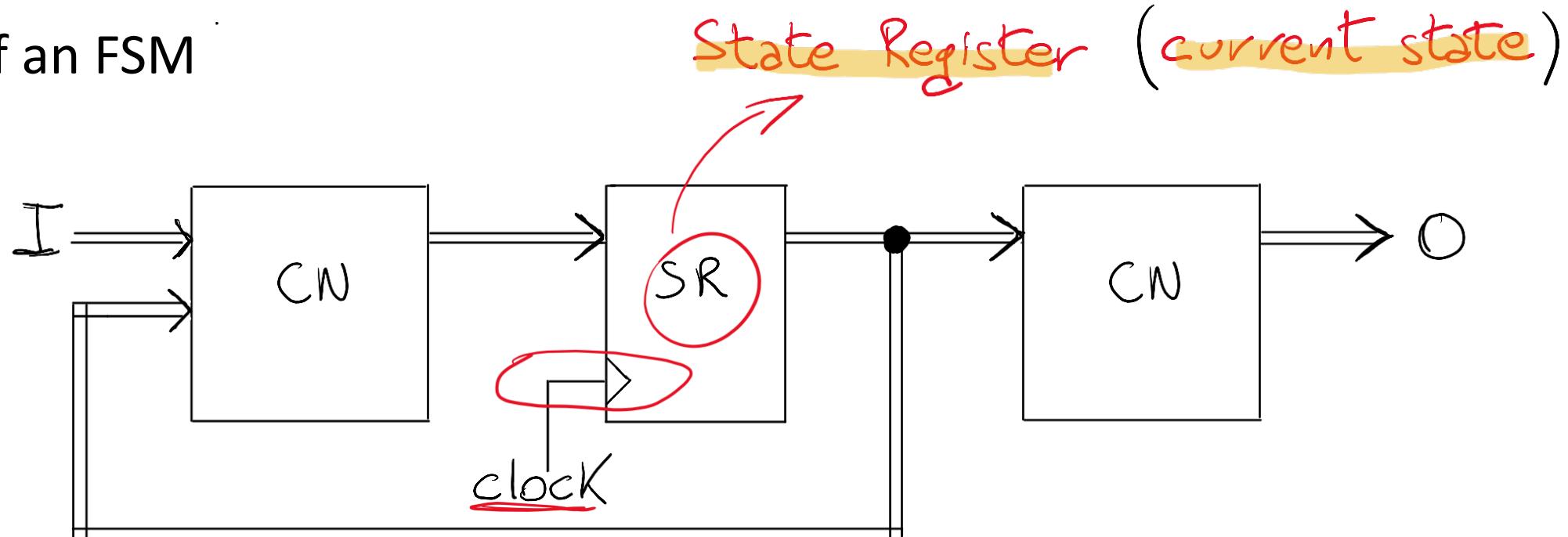


# Finite State Machine (FSM)

- Outline of an FSM

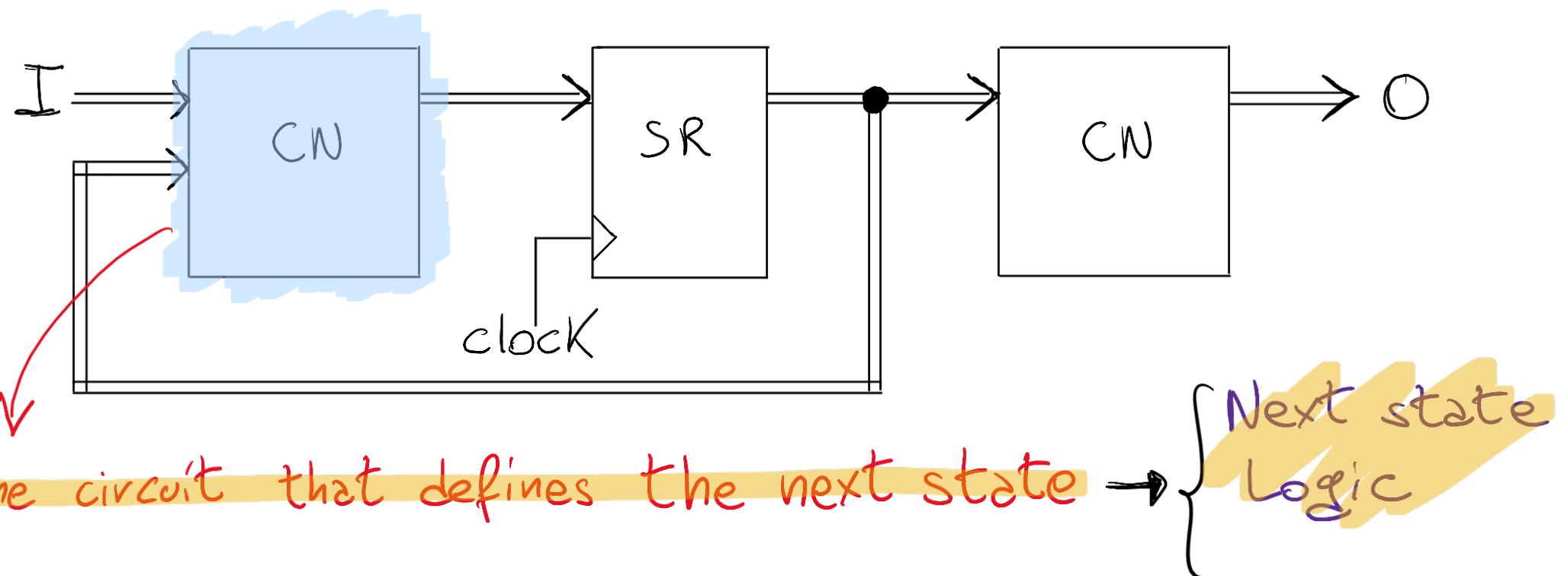

# Finite State Machine (FSM)


- Outline of an FSM

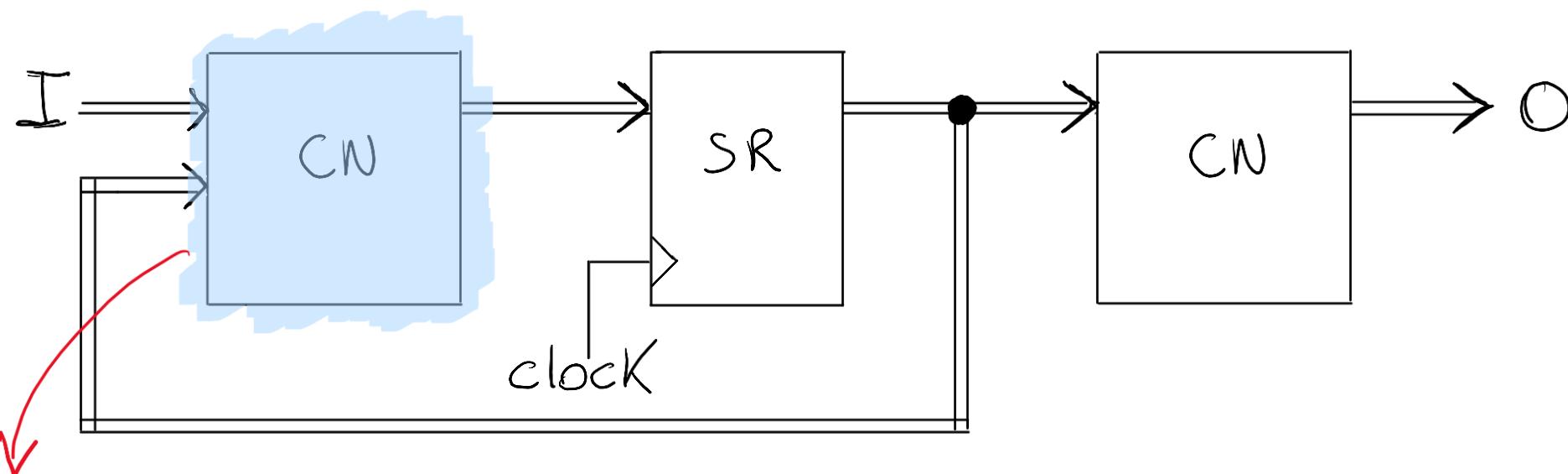

It depends on


# Finite State Machine (FSM)

- Outline of an FSM

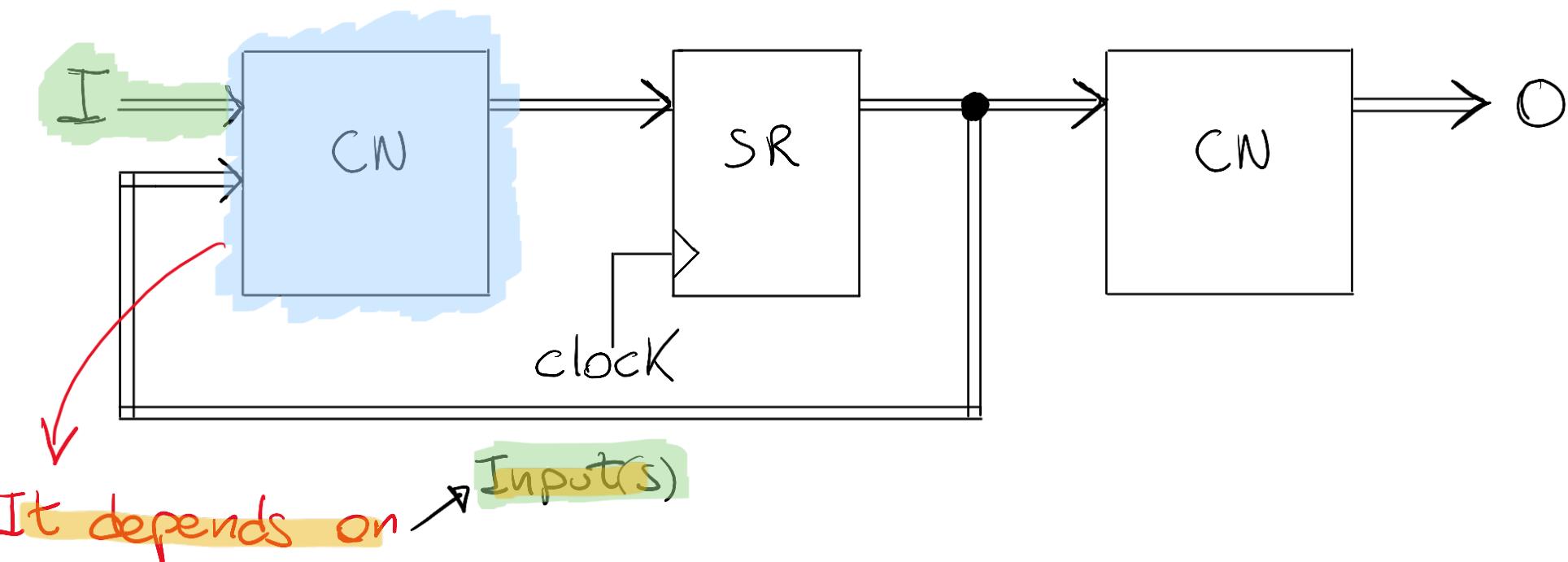


# Finite State Machine (FSM)

- Outline of an FSM

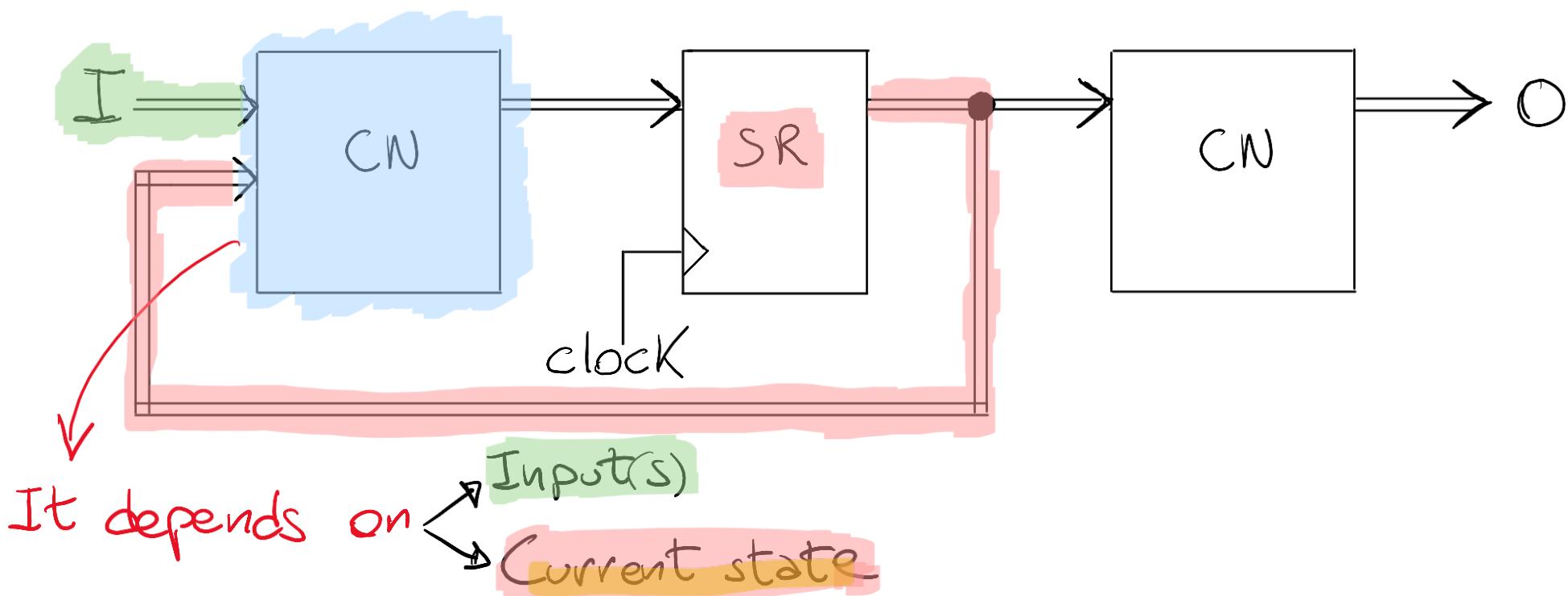

# Finite State Machine (FSM)


- Outline of an FSM

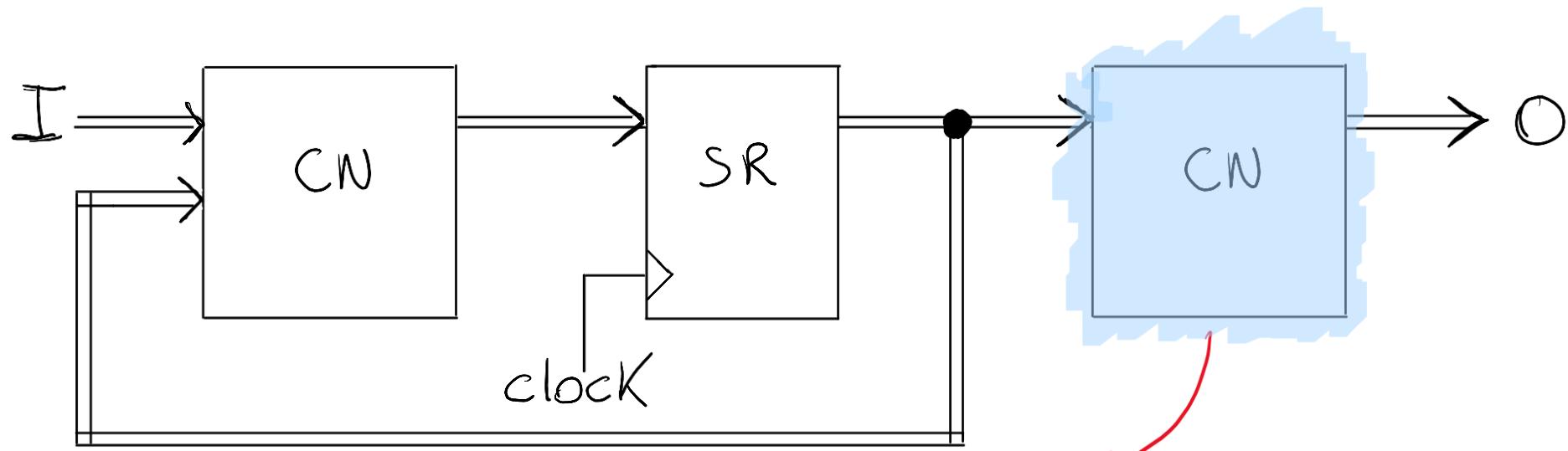

This is the circuit that defines the outputs → Output logic

# Finite State Machine (FSM)


- Outline of an FSM

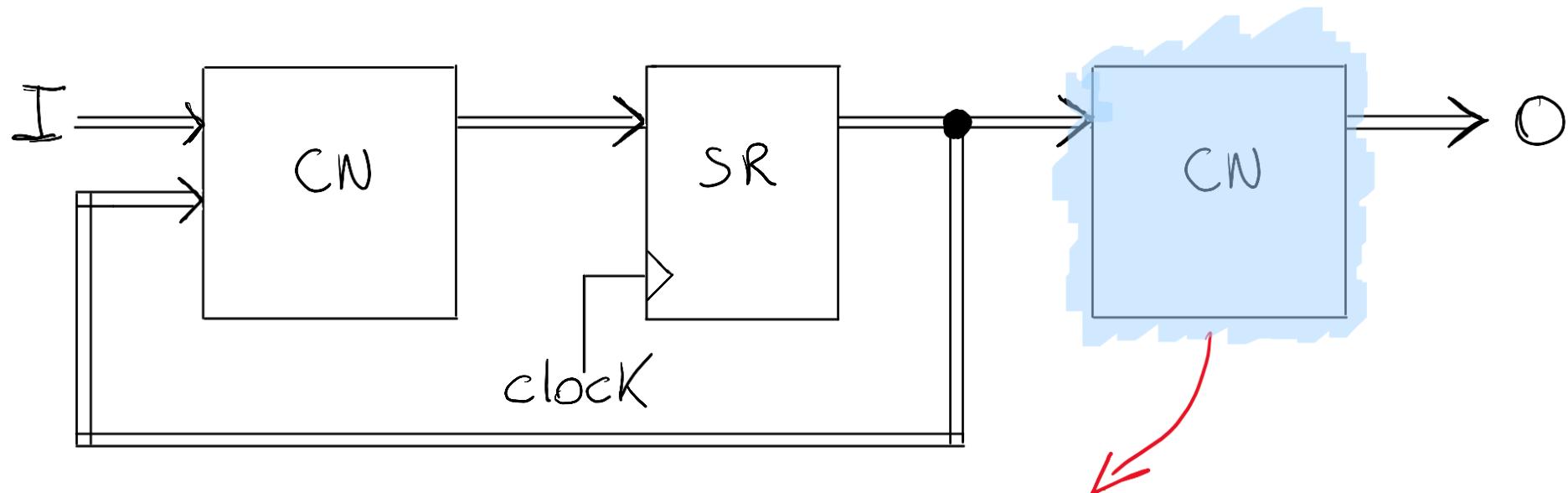

*It depends on*

# Finite State Machine (FSM)


- Outline of an FSM

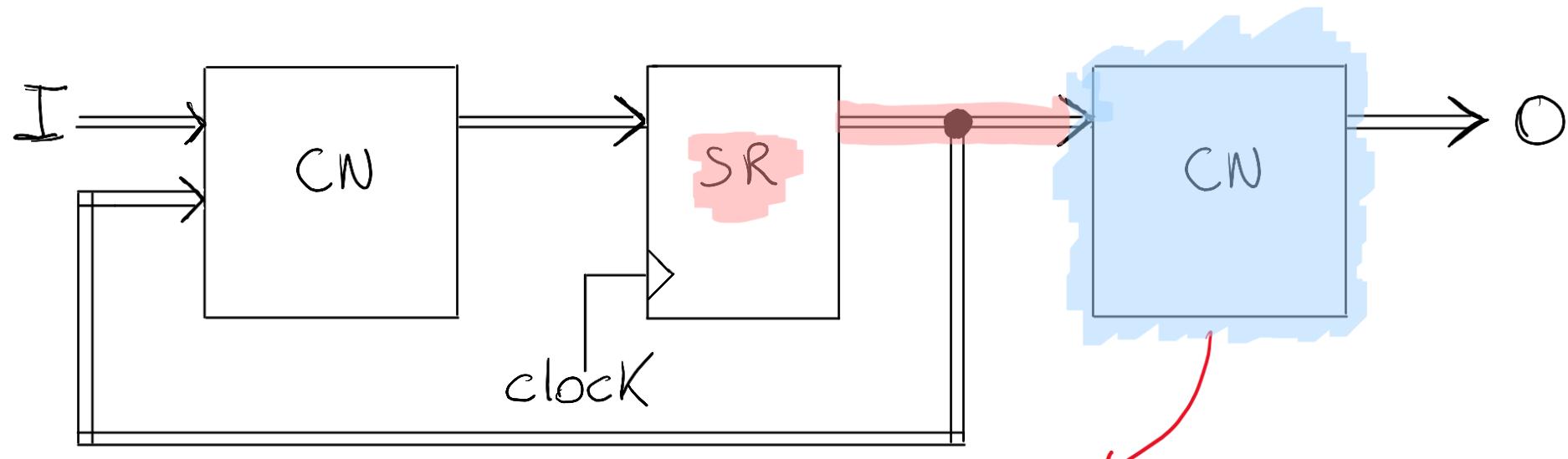

It depends on → **Current state** (ONLY!!!)

# Finite State Machine (FSM)


- Outline of an FSM

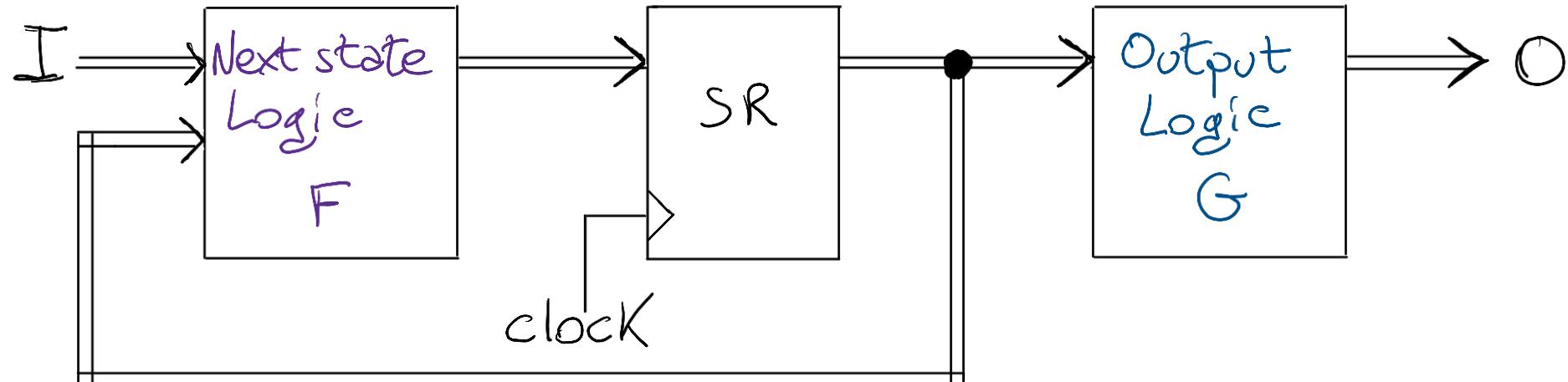
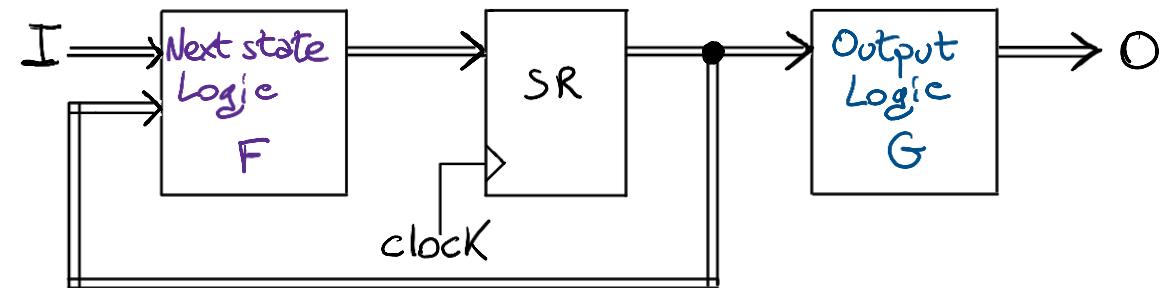
# Finite State Machine (FSM)

- Outline of an FSM

- Next-state =  $F(\text{input}, \text{current state})$




- Output:  $O = G(\text{current state})$ 
  - Moore FSM
  - A Moore FSM is an FSM in which the output depends ONLY on the current state

# Finite State Machine (FSM)

- An FSM can be represented by
  - State diagram
  - State transition table
  - Output transition table
- State and output transition tables can be merged in a unique table

# Finite State Machine (FSM)


- **State diagram (Moore)**

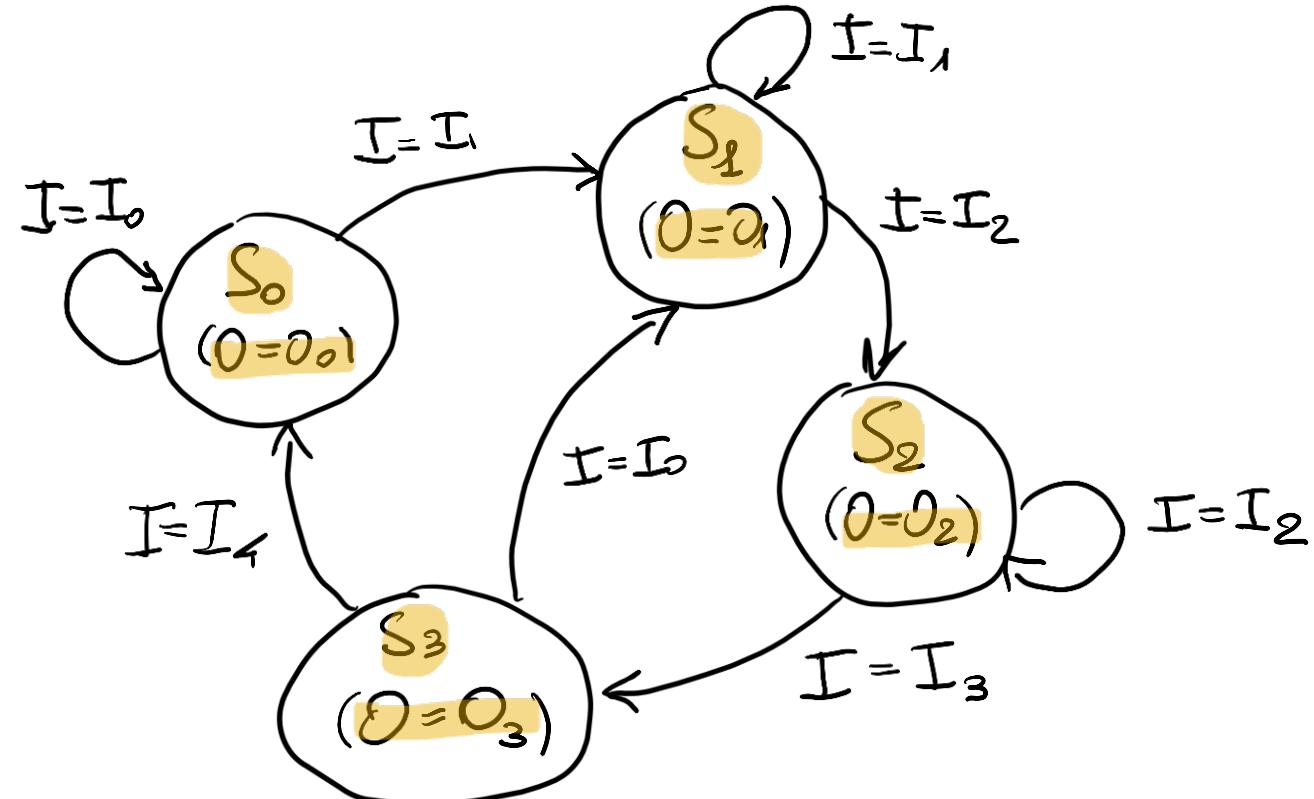

# Finite State Machine (FSM)

- State diagram (Moore)


- State

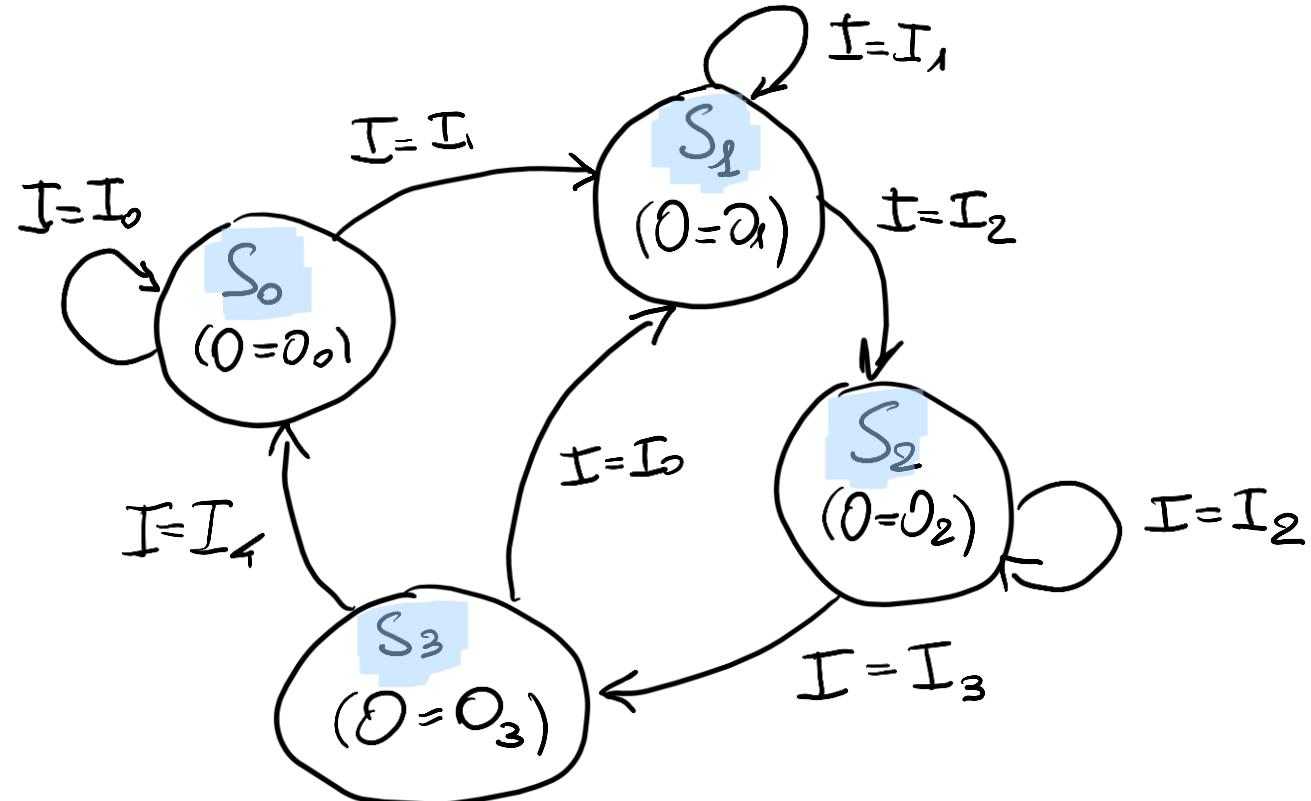

# Finite State Machine (FSM)

- State diagram (Moore)


- State
- Output value  
(per state)

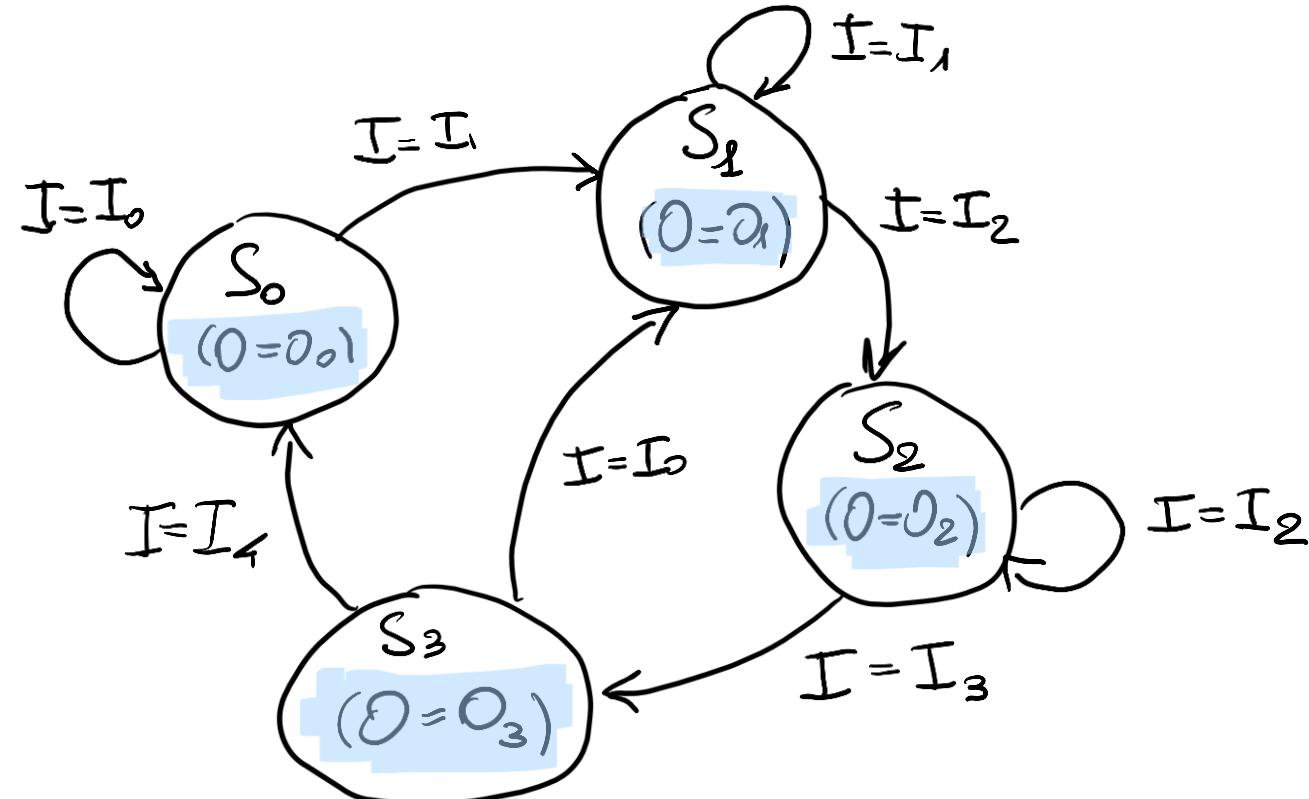
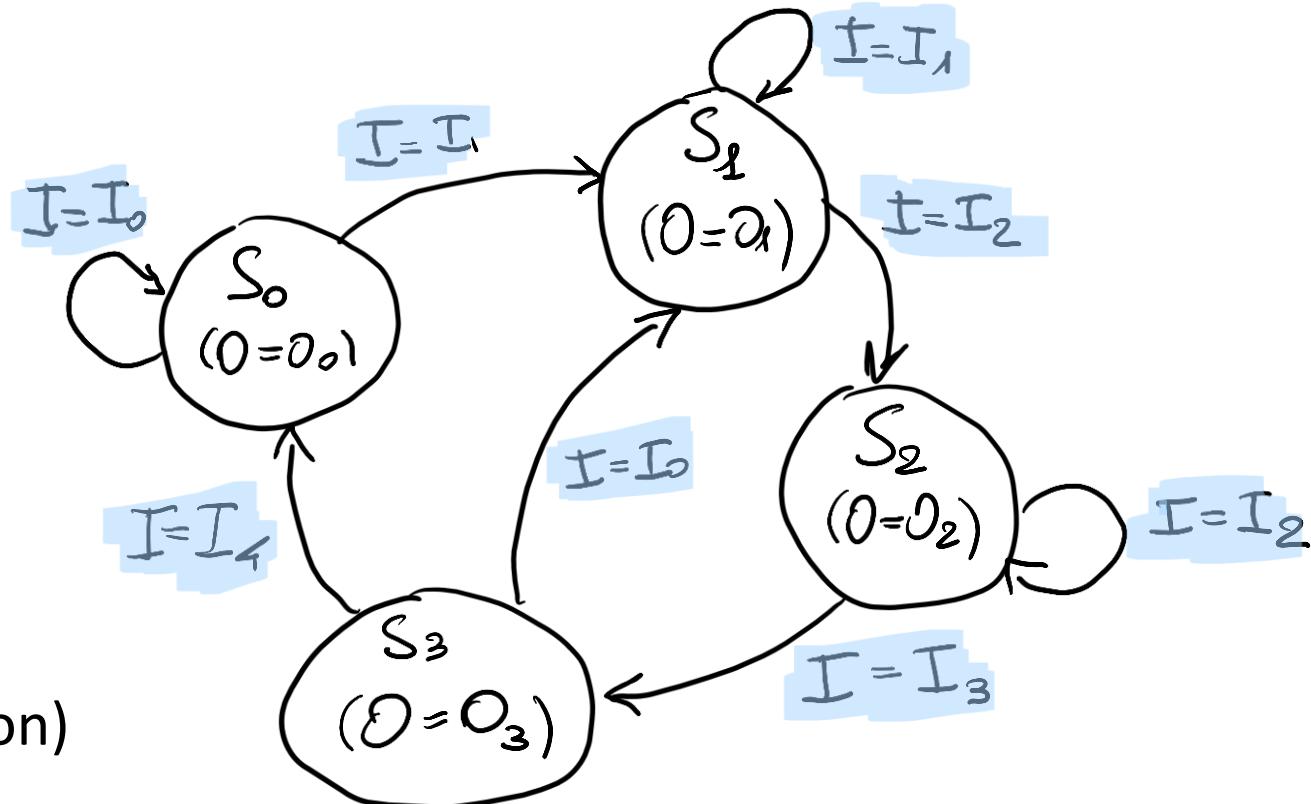
# Finite State Machine (FSM)


- **State diagram (Moore)**

- State
- Output value (per state)
- Input value (trigger for state transition)



# Finite State Machine (FSM)

- State diagram (Moore)

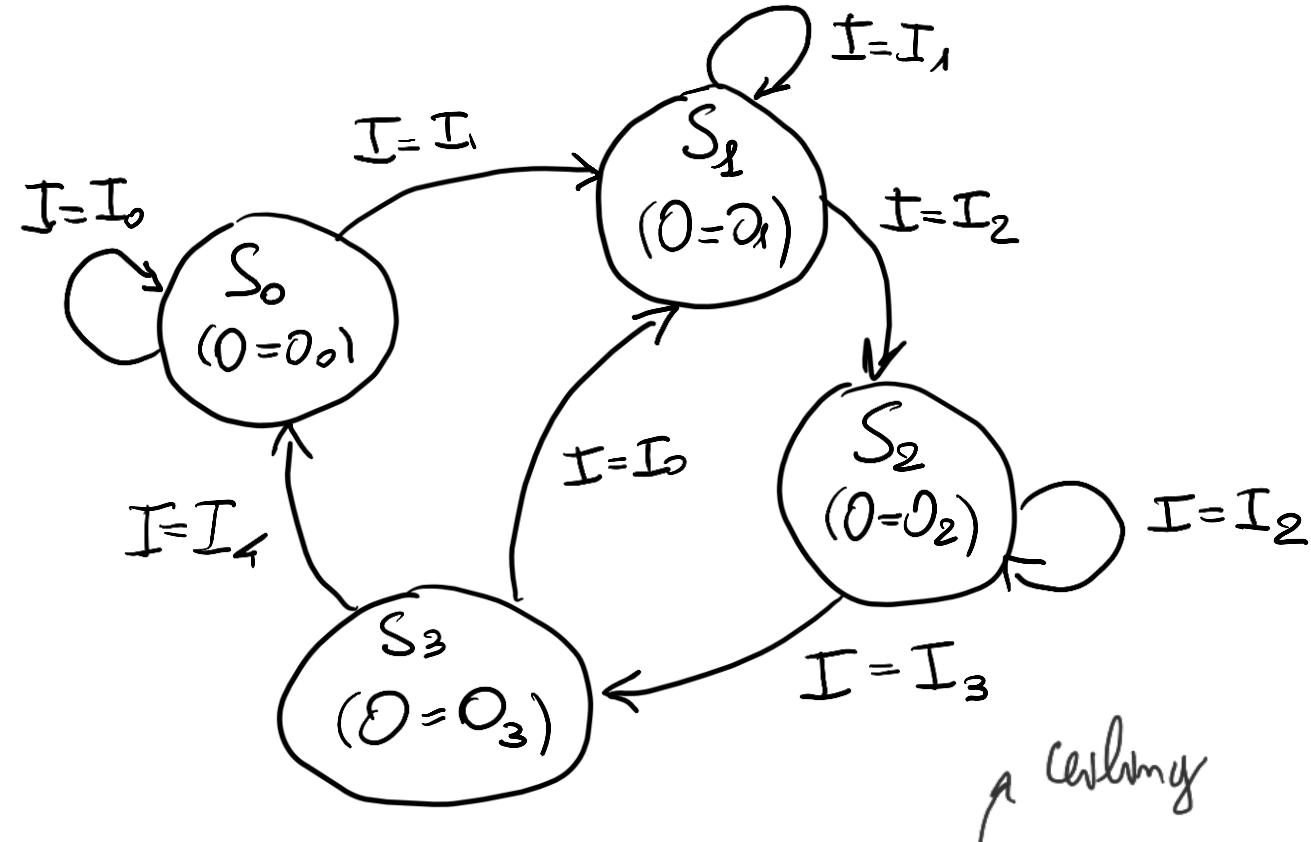

- An FSM with  $N$  states requires a (status) register of  $K = \lceil \log_2(N) \rceil$  bits at least

# Finite State Machine (FSM)

- At least  $K = \lceil \log_2(N) \rceil$ , because other coding style can be used
  - Example: One-hot encoding
    - The binary representation of each state has only one 1; all other bits are 0
    - $N$  states  $\rightarrow K = N$  bits
    - Higher resource consumption (more bits)
    - But higher robustness against disturbance

More bits change so disturbance can be bad (ex: 000  $\rightarrow$  111)

---

One-hot encoding for a 4-state FSM

---

State	SR <sub>0</sub>	SR <sub>1</sub>	SR <sub>2</sub>	SR <sub>3</sub>
S0	1	0	0	0
S1	0	1	0	0
S2	0	0	1	0
S3	0	0	0	1

$SR_i = i^{\text{th}}$  bit of SR (Status Register)

# Finite State Machine (FSM)

- **State transition table (Moore)**

- Input: I (2-bit)

- S = State (current)

- Number of states = 4

- $S^*$  = Next state

S	I			
	00	01	10	11
S0	S0	S0	S1	S1
S1	S2	S1	S2	S2
S2	S0	S3	S0	S3
S3	S1	S3	S0	S1

$S^*$

# Finite State Machine (FSM)

- **Output transition table (Moore)**

- Output: O (3-bit)

- S = State (current)

- Number of states = 4


S	
S0	011
S1	100
S2	110
S3	010
	O

# Finite State Machine (FSM)

- How to set the initial state of FSM?
  - At the power-on of the device/system, the logic value of elements is unpredictable
  - Unless it is addressed with specific techniques
  - Most diffused approach: Power-on Reset (PoR)
    - The main goal of reset is to bring a digital system into a known state!!!
    - Reset signal (and logic) must be added to the FSM circuit

# Finite State Machine (FSM)

- Outline of an FSM

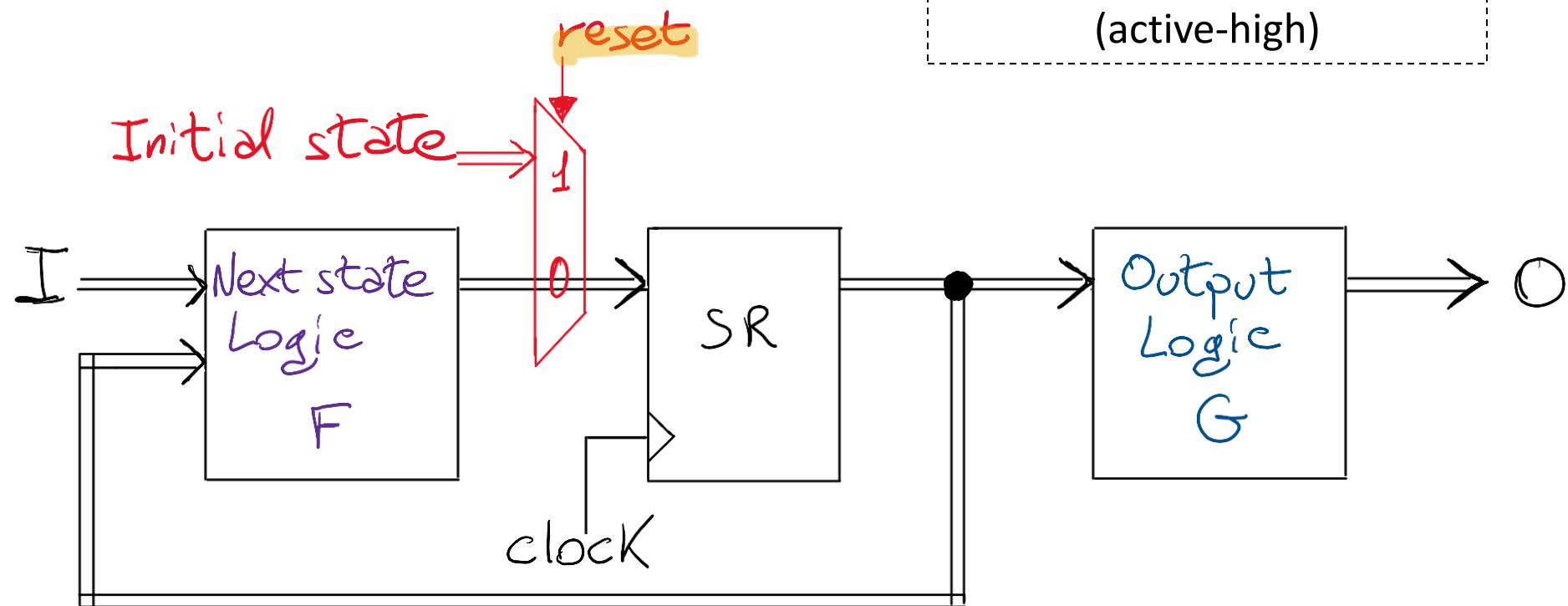


# Finite State Machine (FSM)

- State diagram (Moore)

$S_0 = \text{Initial State}$

$R = \text{reset}$

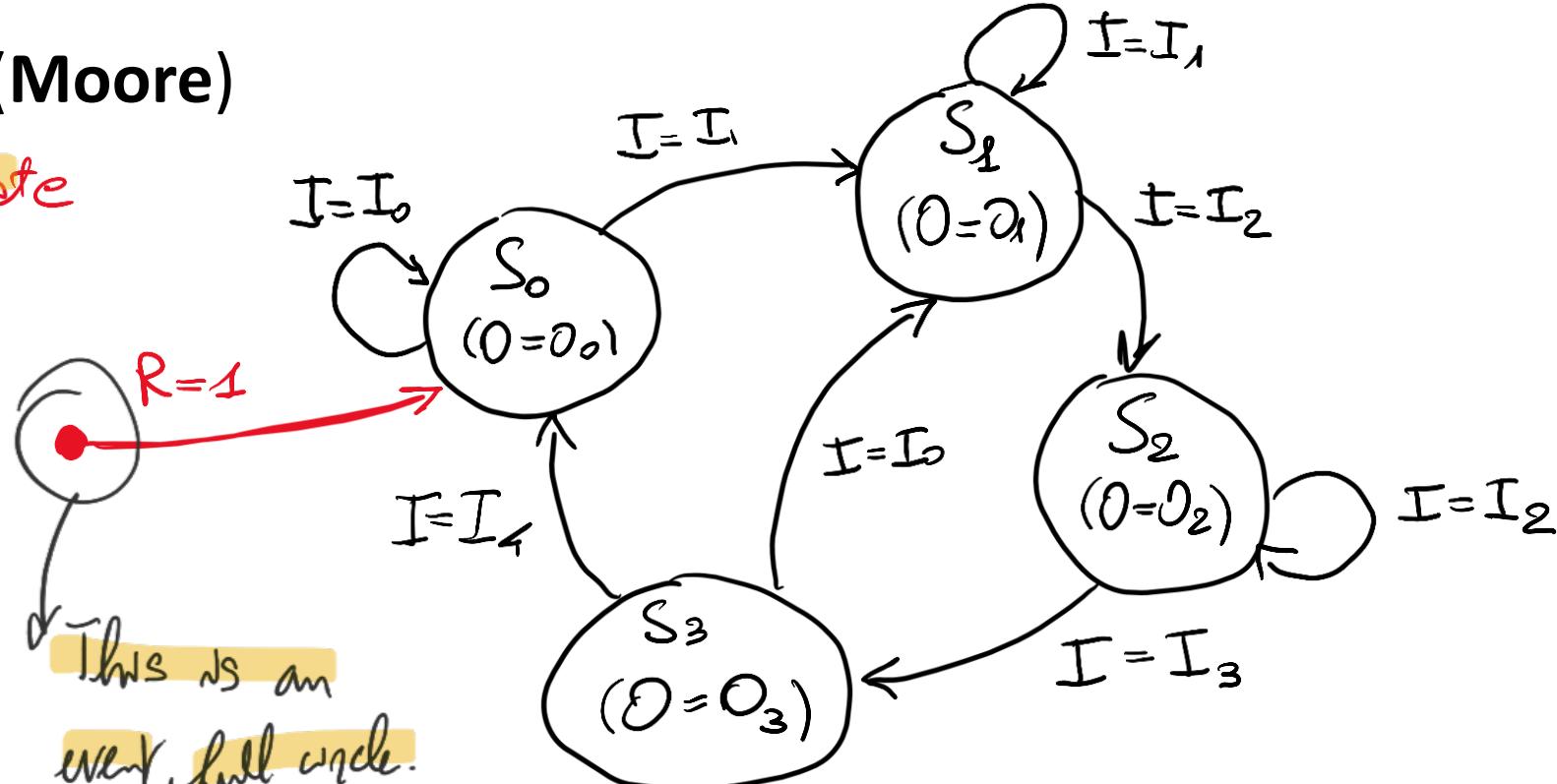


We should add a loop in  $S_0$  for  $R$  because  $R$  is a synchronous input  
 In this case  $I = \text{power on}$ .  $I$  not specified because state doesn't depend on it

# Finite State Machine (FSM)

- State diagram (Moore)

$S_0 = \text{Initial State}$

$R = \text{reset}$

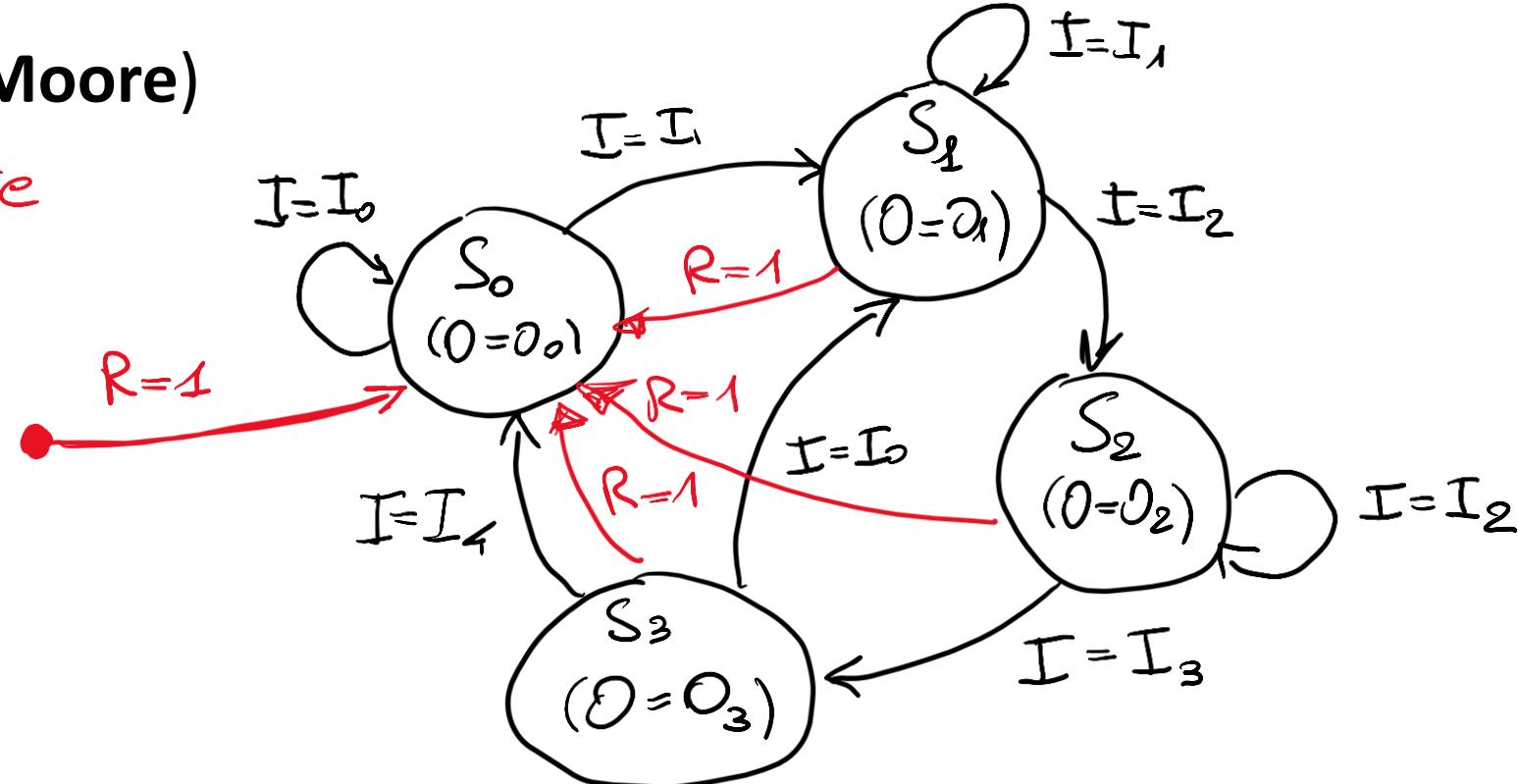


# Finite State Machine (FSM)

- State diagram (Moore)

$S_0 = \text{Initial State}$

$R = \text{reset}$

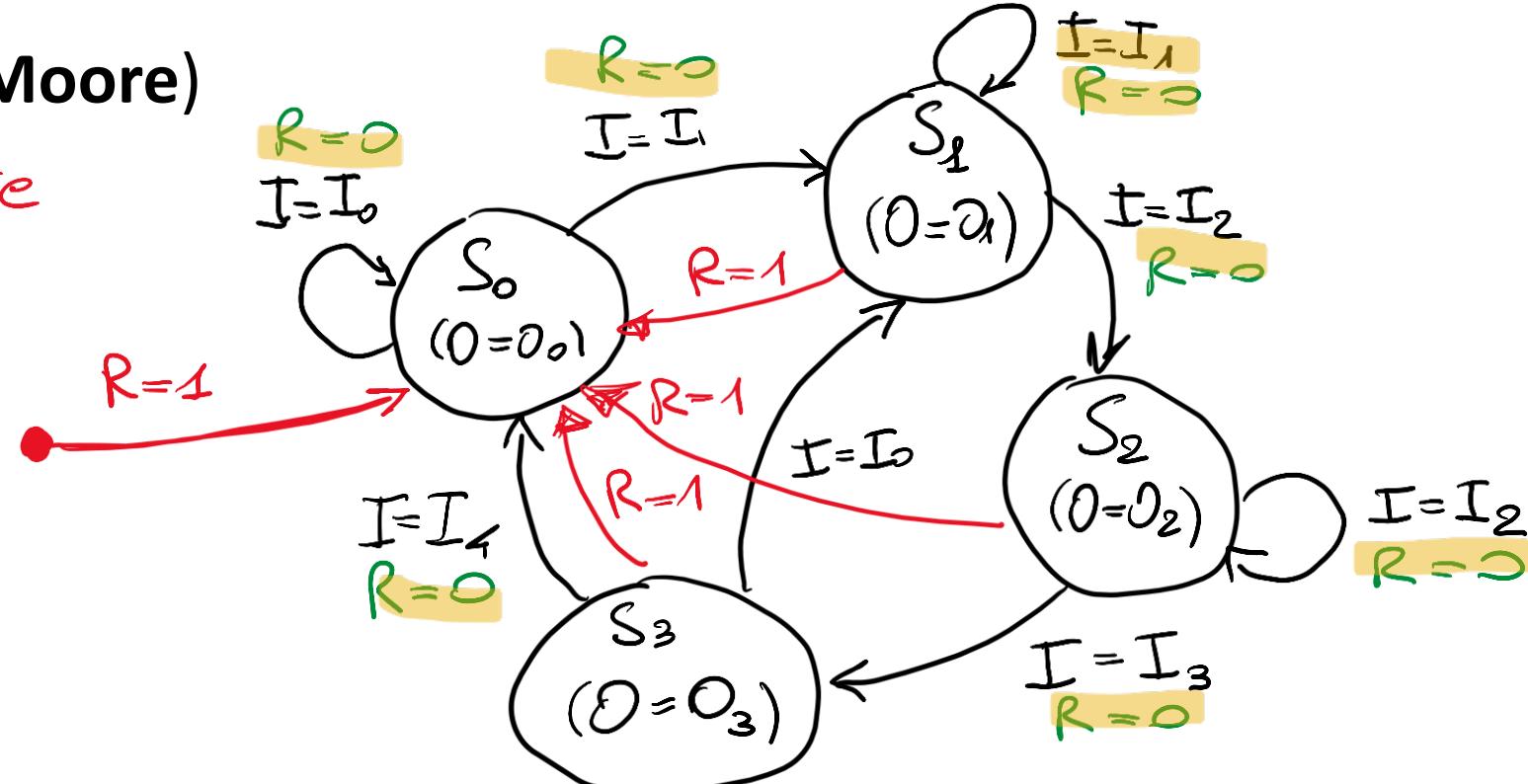

- Also reset signal is an input

# Finite State Machine (FSM)

- **State transition table with reset (Moore)**

- Inputs:
  - I (2-bit)
  - R = Reset (1-bit)

- S = State (current)
  - Number of states = 4
- S0 = Initial state (upon reset)
- S\* = Next state

S	R,I				
	000	001	010	011	1xx
S0	S0	S0	S1	S1	S0
S1	S2	S1	S2	S2	S0
S2	S0	S3	S0	S3	S0
S3	S1	S3	S0	S1	S0


S\*

# Finite State Machine (FSM)

- The Moore architecture is not the only possible architecture for FSM
- Two other architectures exist...
  - ... or better, another main architecture
  - and its modified version to overcome a problem that this second architecture may present


# Finite State Machine (FSM)

- Recall: **Moore FSM**

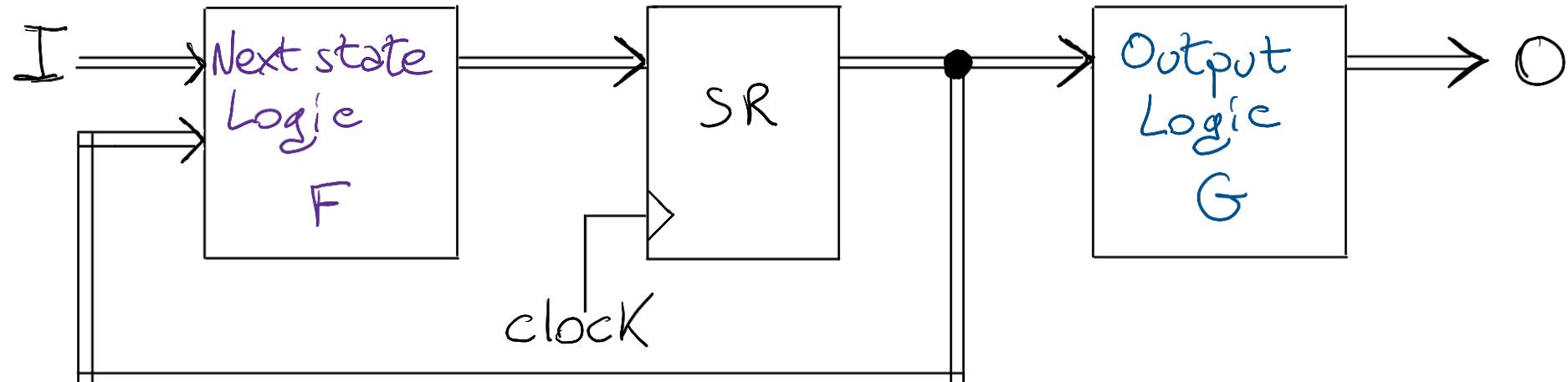

# Finite State Machine (FSM)


- Mealy FSM

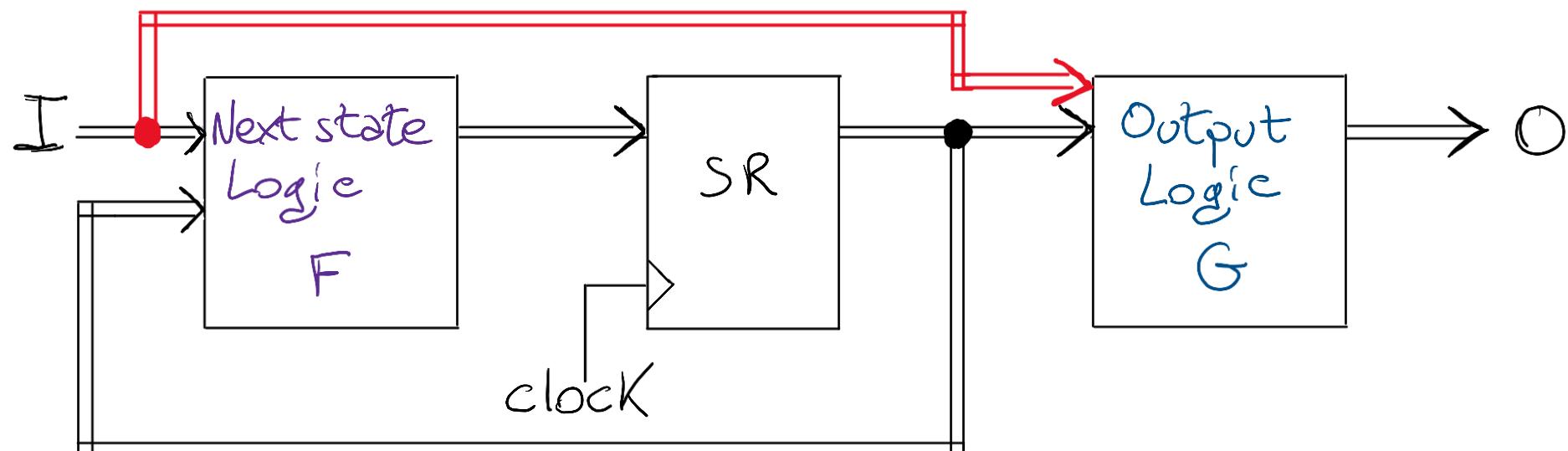
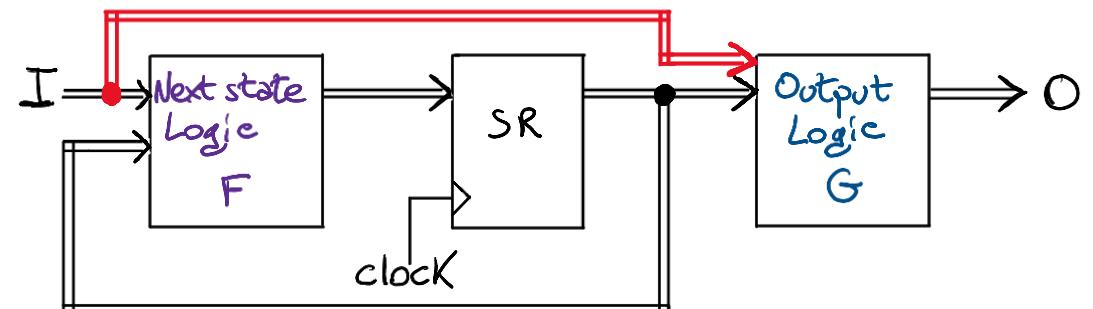
# Finite State Machine (FSM)

- Mealy FSM

- Next-state =  $F(\text{input}, \text{current state})$ 
  - Such as Moore FSM
- Output:  $O = G(\text{input}, \text{current state})$ 
  - A Mealy FSM is an FSM in which the output depends on the current state AND the input




# Finite State Machine (FSM)

Moore FSM

- Next-state =  $F(\text{input}, \text{current state})$


- Output:  $O = G(\text{current state})$

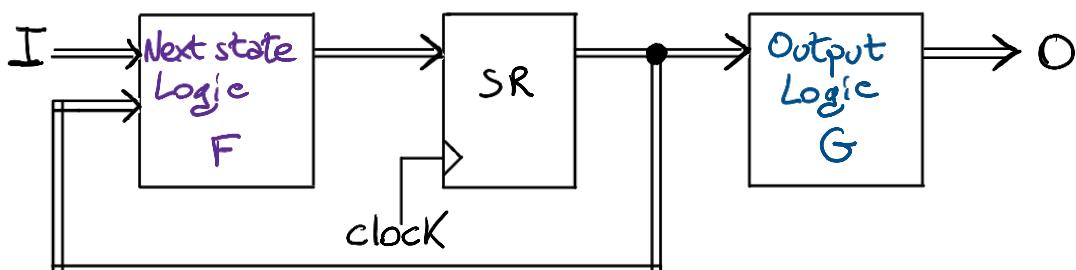

Mealy FSM

- Next-state =  $F(\text{input}, \text{current state})$

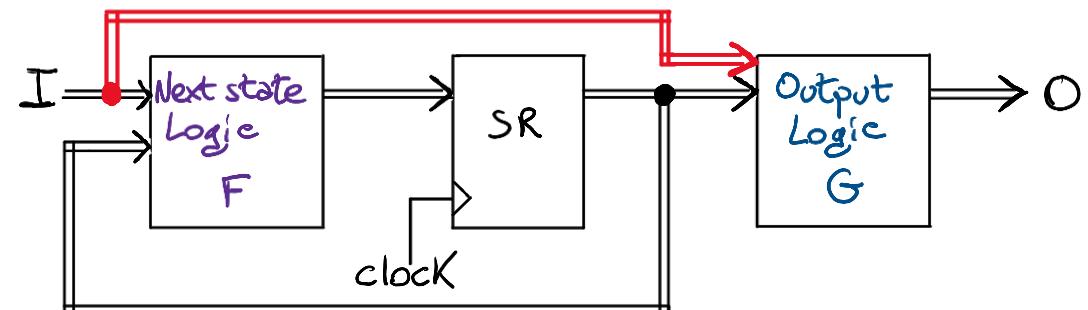
- Output:  $O = G(\text{input, current state})$


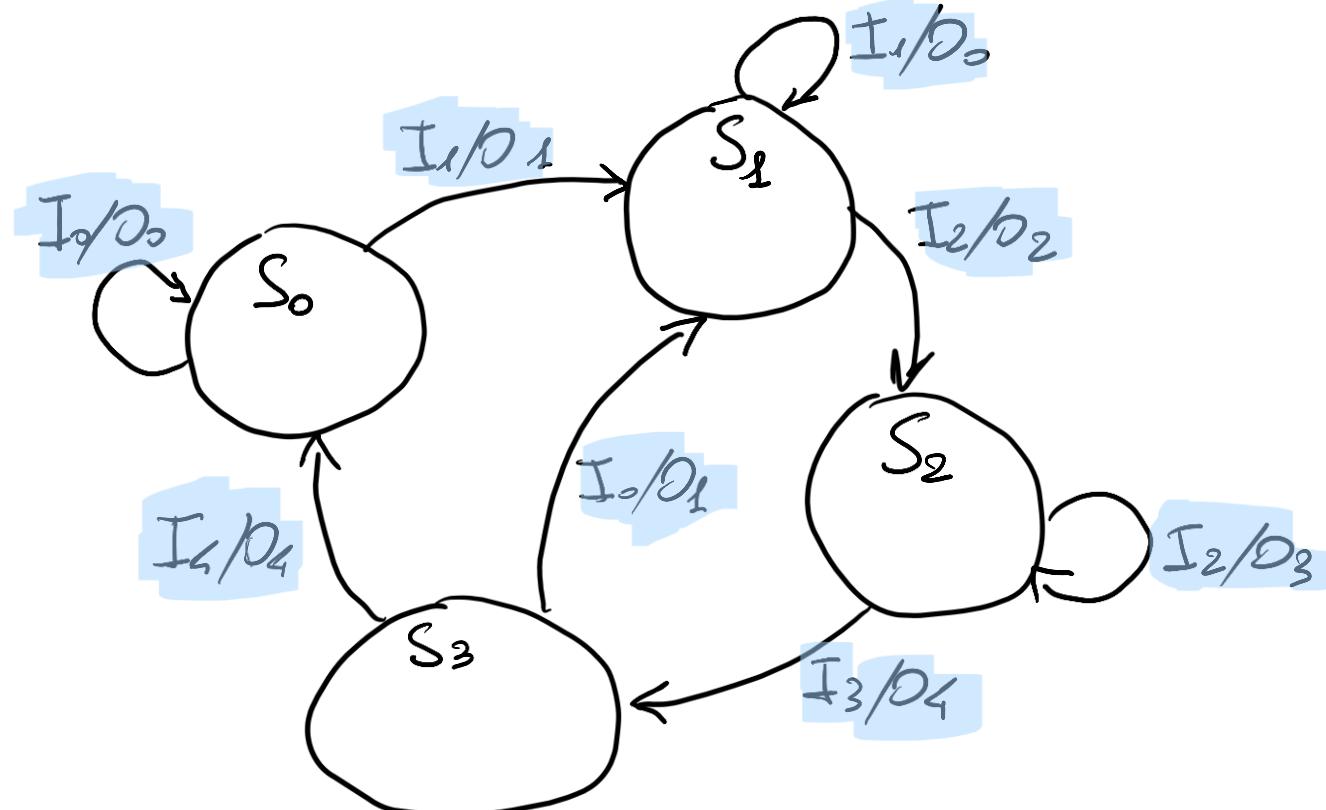
# Finite State Machine (FSM)

- **State diagram (Mealy)**

- **Output is no more associated to the state, but is on the branch (with input)**
  - I/O



# Finite State Machine (FSM)

- State transition table is like the one in Moore's FSM
- Instead, output transition table changes with respect to the one in Moore's FSM, because output depends also on input(s)

# Finite State Machine (FSM)

- **Output transition table (Mealy)**

- Input: I (2-bit)

- S = State (current)

- Number of states = 4

- Output: O (3-bit)

S	I				O
	00	01	10	11	
S0	001	010	010	111	
S1	100	000	011	101	
S2	111	110	101	100	
S3	000	010	110	101	

# Finite State Machine (FSM)

- **State/output transition table (Mealy)**

- Input: I (2-bit)

- S = State (current)

- Number of states = 4

- $S^*$  = Next state

- Output: O (3-bit)

S	I				$S^*, O$
	00	01	10	11	
S0	S0, 001	S0, 010	S1, 010	S1, 111	
S1	S2, 100	S1, 000	S2, 011	S2, 101	
S2	S0, 111	S3, 110	S0, 101	S3, 100	
S3	S1, 000	S3, 010	S0, 110	S1, 101	

# Finite State Machine (FSM)

- Mealy FSM

- Since the output depends on both the current state (i.e. the State Register) and the input(s), the output is asynchronous
  - It does not change (only) on the clock edge as it happens in a Moore FSM
    - In a Moore FSM output is synchronous (with the clock)
  - The output may present spurious transitions, creating problems in some cases

↳ You choose if you need more robustness. If so, you use the registers


# Finite State Machine (FSM)

- Mealy FSM

- Since the output depends on both the current state (i.e. the State Register) and the input(s), the output is asynchronous
  - It does not change (only) on the clock edge as it happens in a Moore FSM
    - In a Moore FSM output is synchronous (with the clock)
  - The output may present spurious transitions, creating problems in some cases
- If so, this problem can be solved by ‘registering’ the output ?
  - I.e., placing a register after the Output logic (G) block
  - In this way the output is again synchronous (with the clock)

# Finite State Machine (FSM)

- Delayed (or pipelined) Mealy FSM

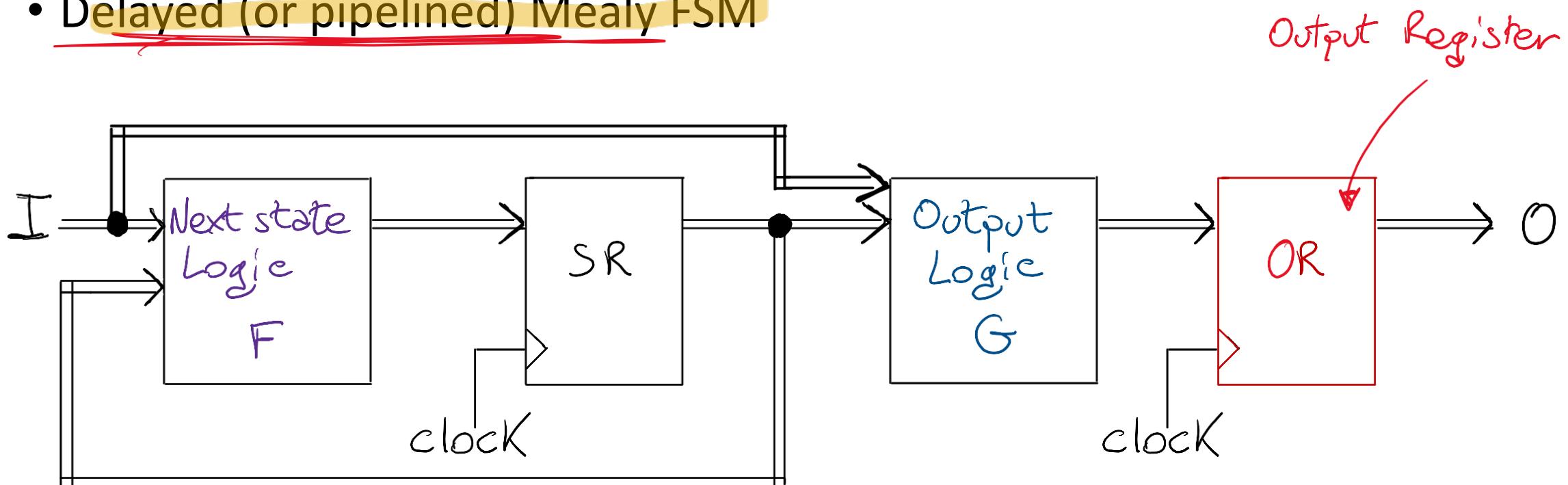

# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim

# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim
  - Input(s)
    - en (1-bit)
    - rst\_n (asynchronous active-low reset)
  - Output(s)
    - out\_code (2-bit)
  - States
    - 4 states: S0, S1, S2, S3
    - 2-bit state register

# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim

- Moore FSM

- S = current state
- S\* = next state

State transition table

S	rst_n, en		
	0x	10	11
S0	S0	S0	S1
S1	S0	S1	S2
S2	S0	S2	S3
S3	S0	S3	S0
S*			


Output transition table

S	out_code
S0	00
S1	01
S2	10
S3	11

# Exercise with SystemVerilog


- Implementation of an FSM and simulation with Modelsim
  - Moore FSM

State diagram

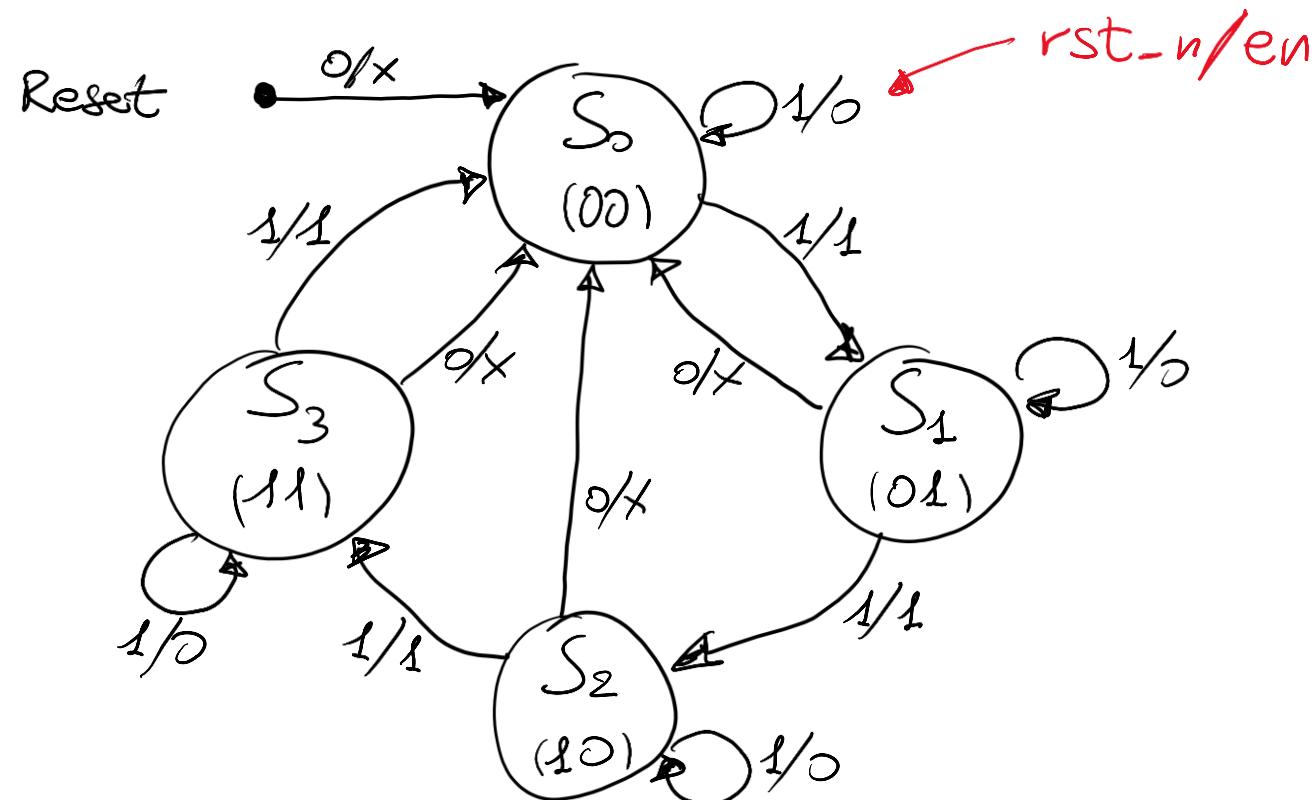

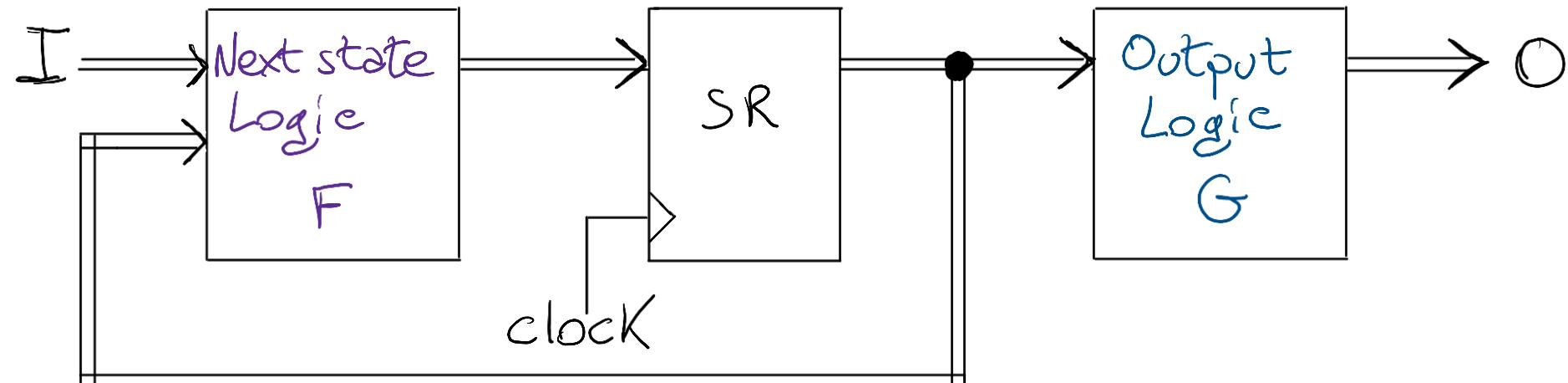
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim


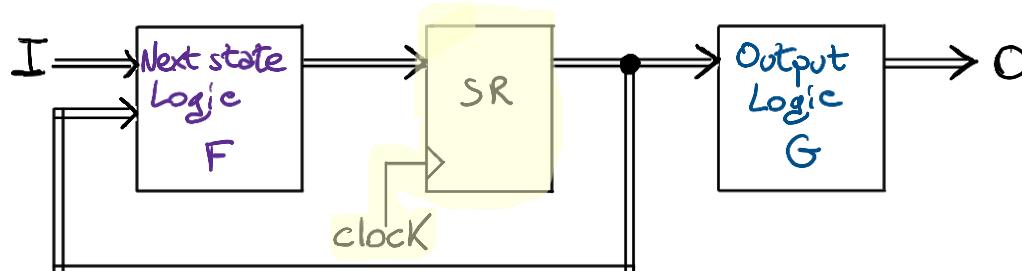
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim




- State register = sequential logic
  - always\_ff block + trigger(s) edge
  - reg signal
  - non-blocking assignment

```
/* Logic signals */
reg [1:0] current_state;

/* State Register (SR) */
always_ff @ (posedge clk or negedge rst_n)
if (!rst_n)
    current_state <= S0;
else
    current_state <= next_state;
```
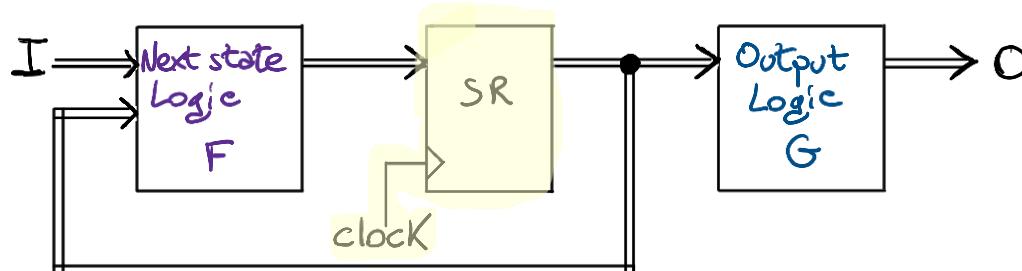
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim




- State register = sequential logic
  - always\_ff block + trigger(s) edge
  - reg signal
  - non-blocking assignment

```
/* Logic signals */
reg [1:0] current_state;

/* State Register (SR) */
① always_ff @ (posedge clk or negedge rst_n)
  if(!rst_n)
    current_state <= S0;
  else
    current_state <= next_state;
```
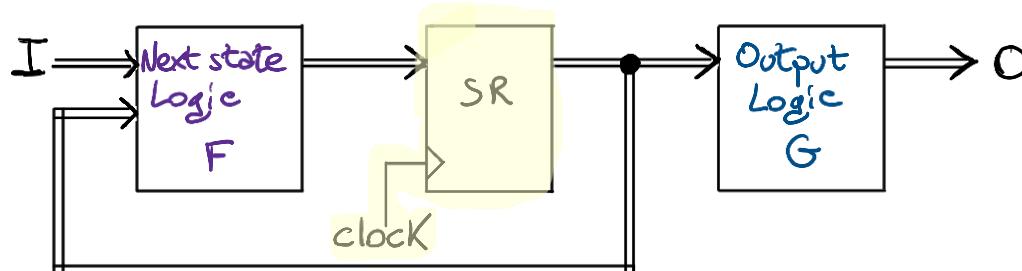
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim




- State register = sequential logic
  - always\_ff block + trigger(s) edge
  - reg signal
  - non-blocking assignment

```
/* Logic signals */  
② reg [1:0] current_state;  
  
/* State Register (SR) */  
① always_ff @ (posedge clk or negedge rst_n)  
    if(!rst_n)  
        current_state <= S0;  
    else  
        current_state <= next_state;
```
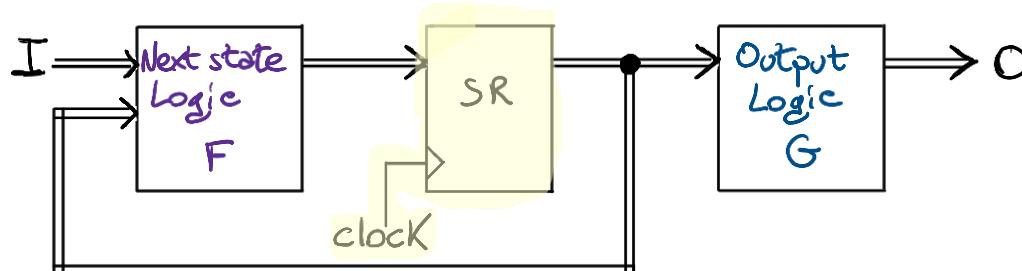
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim



- State register = sequential logic
  - always\_ff block + trigger(s) edge
  - reg signal
  - non-blocking assignment


```

/* Logic signals */
② reg [1:0] current_state;

/* State Register (SR) */
① always_ff @ (posedge clk or negedge rst_n)
  if (!rst_n)
    current_state <= S0;
  else
    current_state <= next_state;
③
  
```
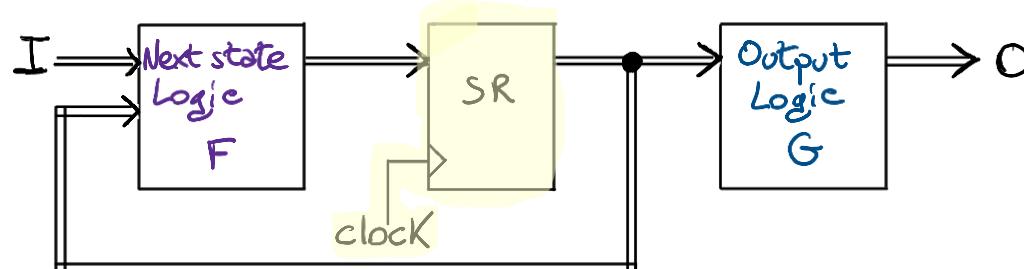
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim




- State register = sequential logic
  - always\_ff block + trigger(s) edge
  - reg signal
  - non-blocking assignment
- Signal internal to the module
  - Must be declared before its usage (in the module body)

```
/* Logic signals */
reg [1:0] current_state;

/* State Register (SR) */
always_ff @ (posedge clk or negedge rst_n)
  if(!rst_n)
    current_state <= S0;
  else
    current_state <= next_state;
```
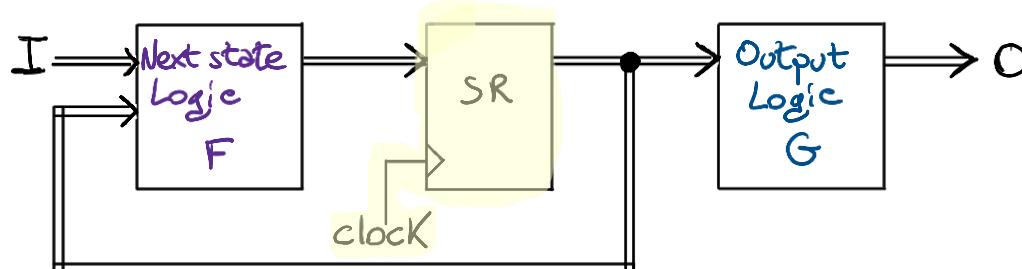
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim



- State register = sequential logic
  - always\_ff block + trigger(s) edge
  - reg signal
  - non-blocking assignment
- Signal internal to the module
  - Must be declared before its usage (in the module body)

```

module fsm (
  /* ports list */
);


/* Logic signals */
reg [1:0] current_state;

/* State Register (SR) */
always_ff @ (posedge clk or negedge rst_n)
  if(!rst_n)
    current_state <= S0;
  else
    current_state <= next_state;

endmodule
  
```
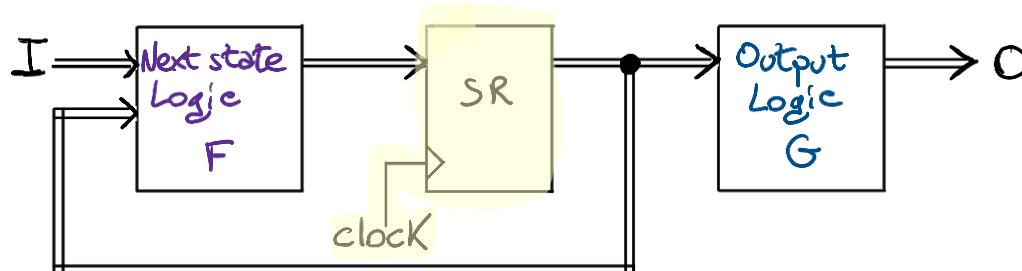
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim



- State register = sequential logic
  - always\_ff block + trigger(s) edge
  - reg signal
  - non-blocking assignment
- Signal internal to the module
  - Must be declared before its usage (in the module body)

```
module fsm (
    /* ports list */
);


/* Logic signals */
reg [1:0] current_state; // ←

/* State Register (SR) */
always_ff @ (posedge clk or negedge rst_n)
if (!rst_n)
    current_state <= S0;
else
    current_state <= next_state;

endmodule
```
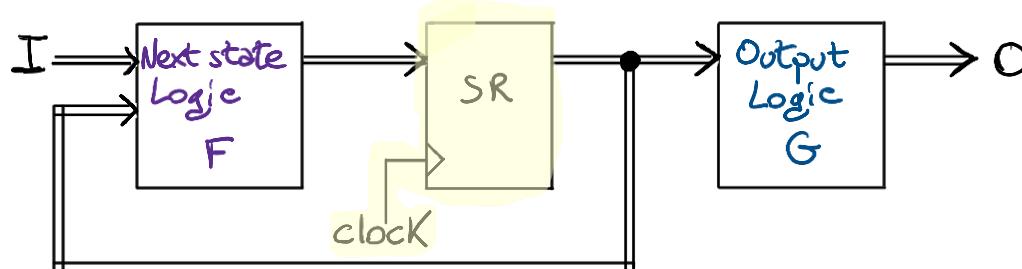
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim



- State register = sequential logic
  - always\_ff block + trigger(s) edge
  - reg signal
  - non-blocking assignment
- Signal internal to the module
  - Must be declared before its usage  
(in the module body)

```

module fsm (
    /* ports list */
);


    /* Logic signals */
    reg [1:0] current_state; ←

    /* State Register (SR) */
    always_ff @ (posedge clk or negedge rst_n)
        if (!rst_n)
            →current_state <= S0;
        else
            →current_state <= next_state;

endmodule
  
```
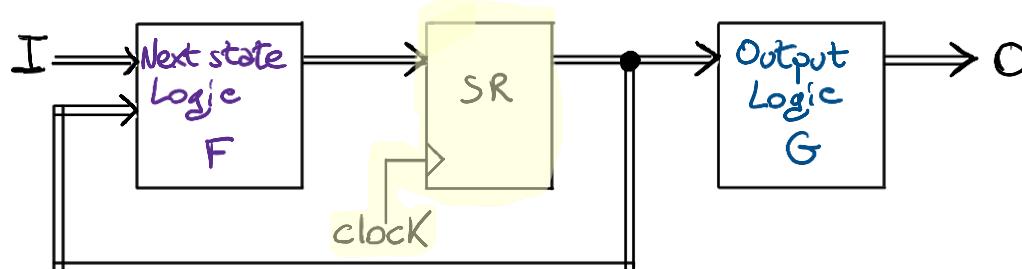
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim



- State register = sequential logic
  - always\_ff block + trigger(s) edge
  - reg signal
  - non-blocking assignment
- Signal internal to the module
  - Must be declared before its usage**  
(in the module body)

```

module fsm (
  /* ports list */
);

  /* Logic signals */
  reg [1:0] current_state; ←


  /* State Register (SR) */
  always_ff @ (posedge clk or negedge rst_n)
    if (!rst_n)
      → current_state <= S0;
    else
      → current_state <= next_state;

endmodule

```
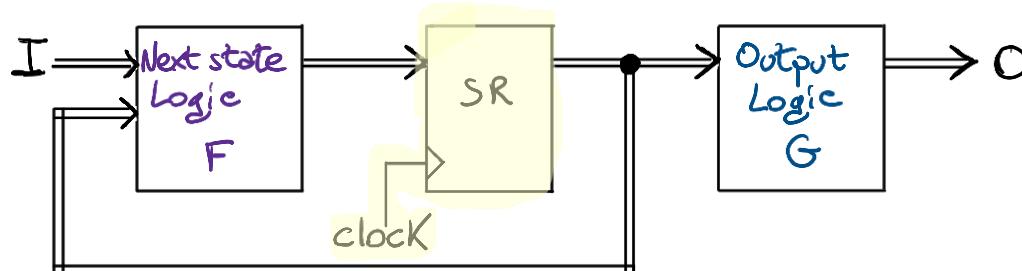
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim




- States can be coded using **labels**

```
/* Logic signals */
reg [1:0] current_state;


/* State Register (SR) */
always_ff @ (posedge clk or negedge rst_n)
  if(!rst_n)
    current_state <= S0;
  else
    current_state <= next_state;
```
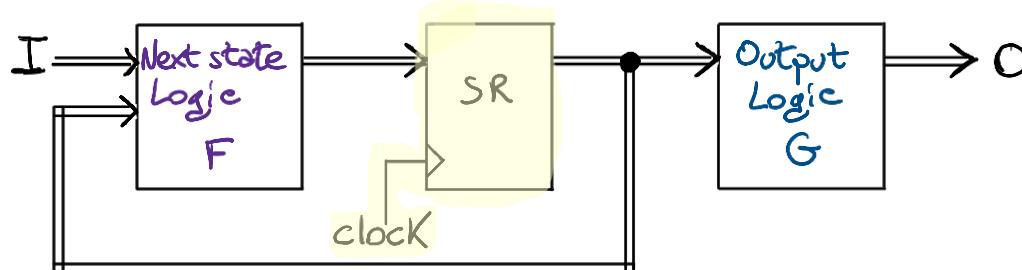
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim



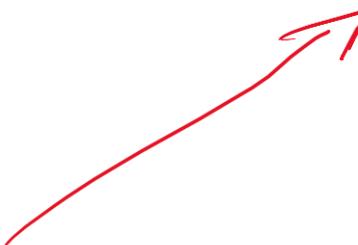- States can be coded using labels
  - Local parameters
    - Syntax: **localparam <name> = <constant value>;**
  - Again: declare before usage!!!




```
/* State labels */
localparam S0 = 2'b00;
localparam S1 = 2'b01;
localparam S2 = 2'b10;
localparam S3 = 2'b11;

/* Logic signals */
reg [1:0] current_state;

/* State Register (SR) */
always_ff @ (posedge clk or negedge rst_n)
  if(!rst_n)
    current_state <= S0;
  else
    current_state <= next_state;
```
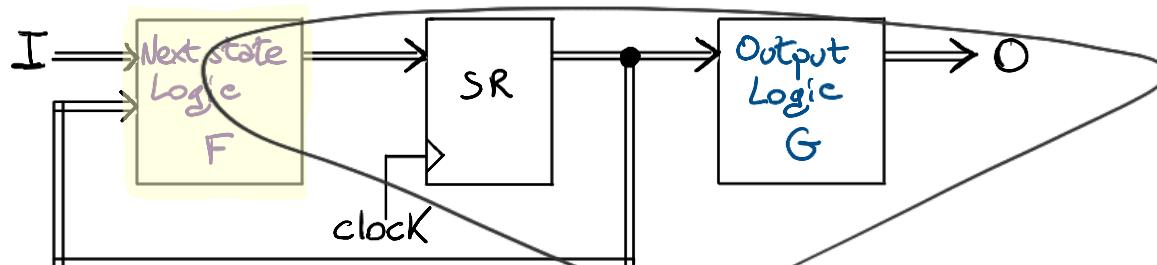
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim



- The always\_ff block includes the dependence on the asynchronous active-low reset for the next state
  - Such signal can be omitted in the description of F

```


/* State labels */
localparam S0 = 2'b00;
localparam S1 = 2'b01;
localparam S2 = 2'b10;
localparam S3 = 2'b11;

/* Logic signals */
reg [1:0] current_state;

/* State Register (SR) */
always_ff @ (posedge clk or negedge rst_n)
  if(!rst_n)
    current_state <= S0;
  else
    current_state <= next_state;
  
```
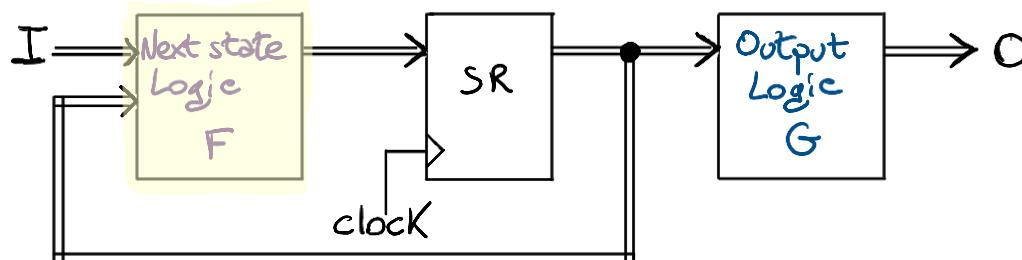
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim



- The `always_ff` block includes the dependence on the asynchronous active-low reset for the next state
  - Such signal can be omitted in the description of F
- F (next-state logic) is combinational
  - Case statement can be very useful, so ...
    - `always_comb`
    - blocking assignment on `reg` signal

*always comb = blocking assignment*

That works  
on reg though

```


/* State labels */
localparam S0 = 2'b00;
localparam S1 = 2'b01;
localparam S2 = 2'b10;
localparam S3 = 2'b11;

/* Logic signals */
reg [1:0] current_state;

/* State Register (SR) */
always_ff @ (posedge clk or negedge rst_n)
  if (!rst_n)
    current_state <= S0;
  else
    current_state <= next_state;
  
```
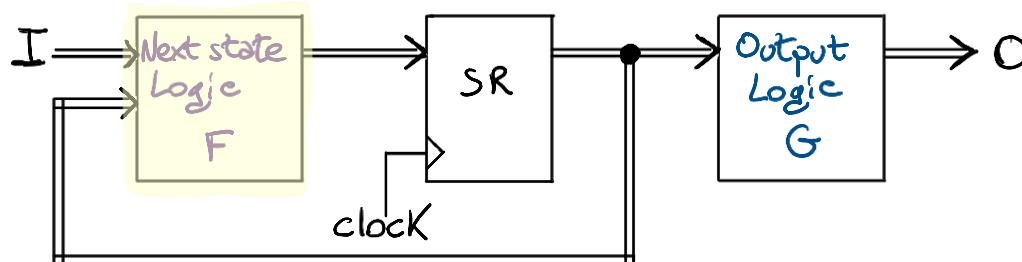
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim



- The `always_ff` block includes the dependence on the asynchronous active-low reset for the next state
  - Such signal can be omitted in the description of F
- F (next-state logic) is combinational
  - Case statement can be very useful, so ...
    - `always_comb`
    - blocking assignment on `reg` signal

```


/* State labels */
localparam S0 = 2'b00;
localparam S1 = 2'b01;
localparam S2 = 2'b10;
localparam S3 = 2'b11;

/* Logic signals */
reg [1:0] current_state;
→ reg [1:0] next_state;

/* State Register (SR) */
always_ff @ (posedge clk or negedge rst_n)
  if(!rst_n)
    current_state <= S0;
  else
    current_state <= next_state;
  
```
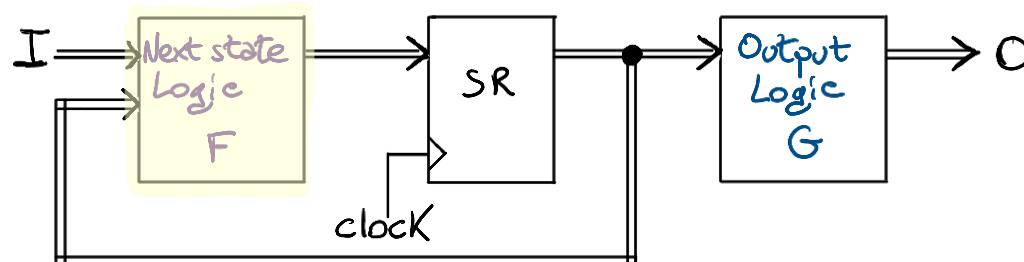
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim




```
/* Next-state logic (F) */
always_comb
```

```
case (current_state)
  S0: next_state = en ? S1 : S0;
  S1: next_state = en ? S2 : S1;
  S2: next_state = en ? S3 : S2;
  S3: next_state = en ? S0 : S3;
endcase
```

- The always\_ff block includes the dependence on the asynchronous active-low reset for the next state
  - Such signal can be omitted in the description of F
- F (next-state logic) is combinational
  - Case** statement can be very useful, so ...
    - always\_comb**
    - blocking assignment** on reg signal
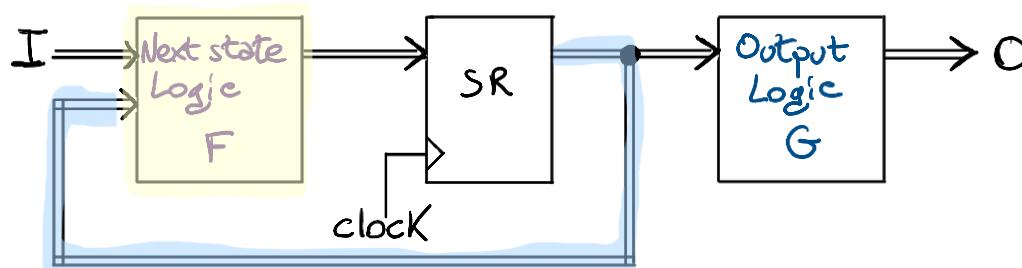
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim




- The always\_ff block includes the dependence on the asynchronous active-low reset for the next state
  - Such signal can be omitted in the description of F
- F (next-state logic) is combinational
  - Case statement can be very useful, so ...
    - always\_comb
    - blocking assignment on reg signal

dependence on the current state

```
/* Next-state logic (F) */  
always_comb  
  
case (current_state)  
S0: next_state = en ? S1 : S0;  
S1: next_state = en ? S2 : S1;  
S2: next_state = en ? S3 : S2;  
S3: next_state = en ? S0 : S3;  
endcase
```
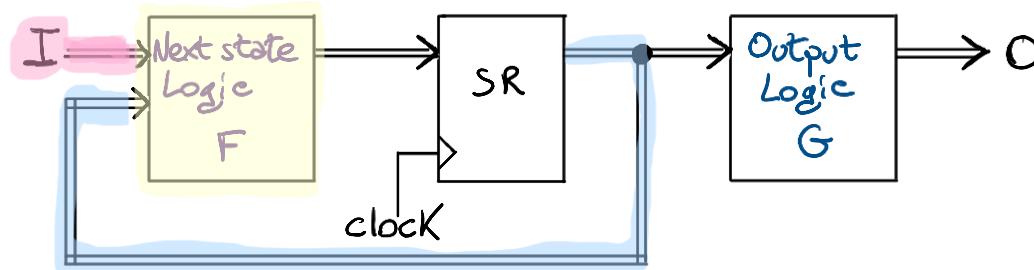
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim



- The always\_ff block includes the dependence on the asynchronous active-low reset for the next state
  - Such signal can be omitted in the description of F
- F (next-state logic) is combinational
  - Case statement can be very useful, so ...
    - always\_comb
    - blocking assignment on reg signal

dependence on the current state

```


/* Next-state logic (F) */
always_comb
  case (current_state)
    S0: next_state = en ? S1 : S0;
    S1: next_state = en ? S2 : S1;
    S2: next_state = en ? S3 : S2;
    S3: next_state = en ? S0 : S3;
  endcase

```

dependence on inputs
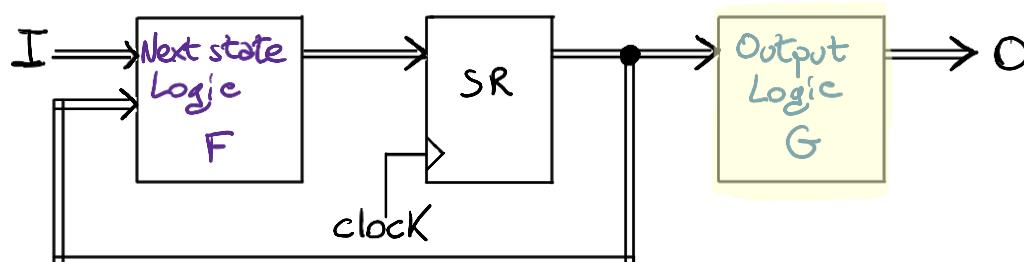
# Exercise with SystemVerilog


- Implementation of an FSM and simulation with Modelsim



- G (output logic) can be implemented in the same way as F
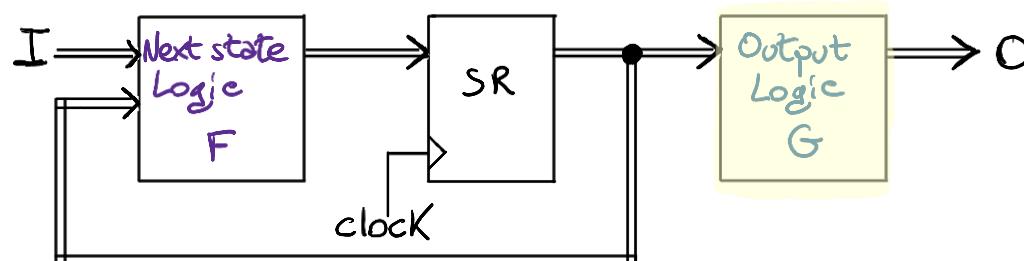
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim




```
/* Output logic (G) */
always_comb
```

```
case (current_state)
S0: out_code = 2'd0;
S1: out_code = 2'd1;
S2: out_code = 2'd2;
S3: out_code = 2'd3;
endcase
```

- G (output logic) can be implemented in the same way as F
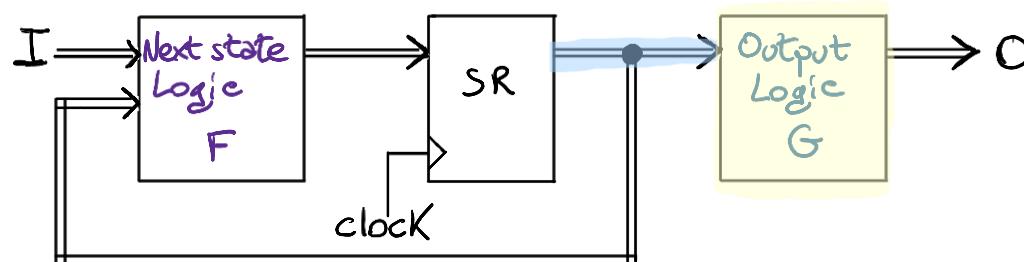
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim



- G (output logic) can be implemented in the same way as F
  - It depends only on the current state


dependence on the current state

```
/* Output logic (G) */  
always_comb
```

```
case (current_state)  
S0: out_code = 2'd0;  
S1: out_code = 2'd1;  
S2: out_code = 2'd2;  
S3: out_code = 2'd3;  
endcase
```
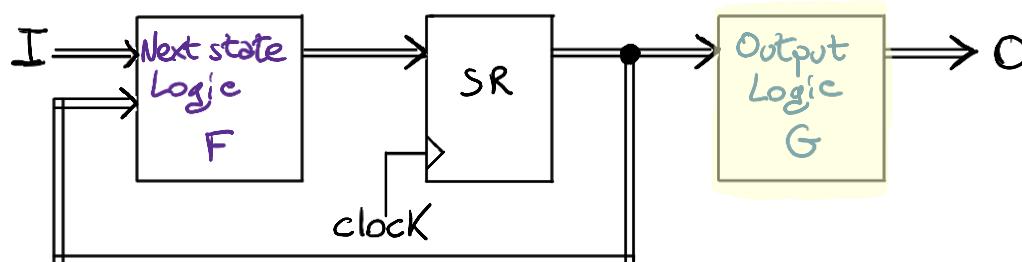
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim




- G (output logic) can be implemented in the same way as F
  - It depends only on the current state
  - Output (out\_code) must be a **reg**

```
module fsm (
    input clk,
    input rst_n,
    input en,
    output reg [1:0] out_code
);
```
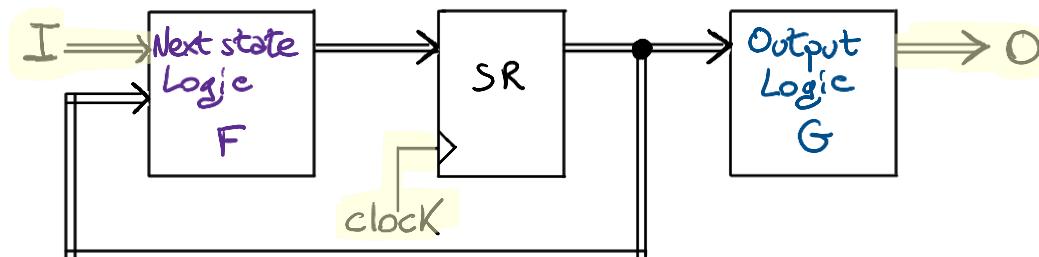
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim




- List of ports (and module declaration)

```
module fsm (
    input clk,
    input rst_n,
    input en,
    ,output reg [1:0] out_code
);
```

Every assignment is always REG in blocking assignment
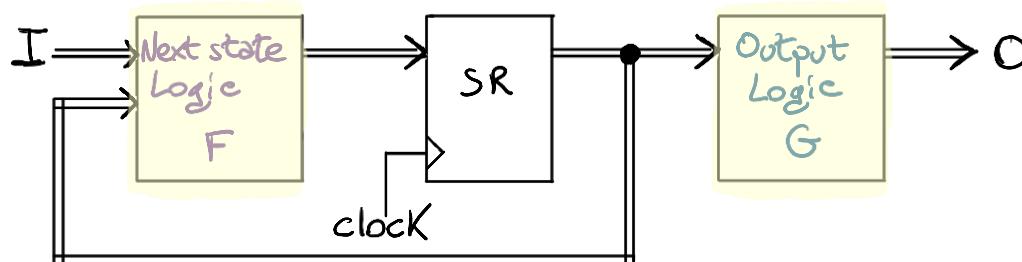
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim



- F and G can also be merged together

```
/* Next-state/Output logic (F/G) */
always_comb

  case(current_state)

    S0: begin
      out_code   = 2'd0;
      next_state = en ? S1 : S0;
    end

    S1: begin
      out_code   = 2'd1;
      next_state = en ? S2 : S1;
    end


    S2: begin
      out_code   = 2'd2;
      next_state = en ? S3 : S2;
    end

    S3: begin
      out_code   = 2'd3;
      next_state = en ? S0 : S3;
    end

  endcase
```
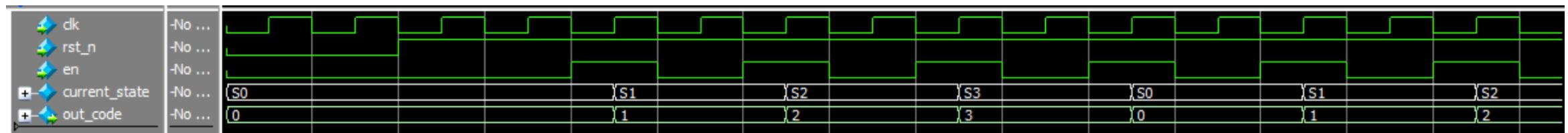
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim
  - You can find all the files about this exercise in the dedicated folder on the Team of the course
    - File > Electronics Systems module > Crocetti > Exercises > 2.4
  - Try to simulate on your own




# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim
  - You can find all the files about this exercise in the dedicated folder on the Team of the course
    - File > Electronics Systems module > Crocetti > Exercises > 2.4
  - Try to simulate on your own
  - However, I also included two .do files to automate the waveform and the simulation
    - wave.do and sim.do
    - Refer to README.txt file
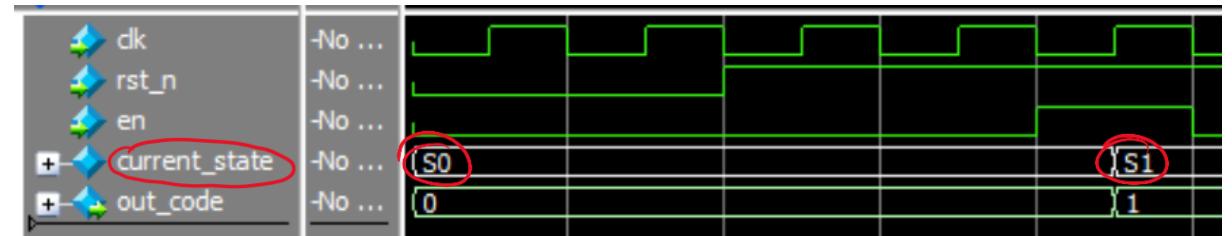
# Exercise with SystemVerilog

- Implementation of an FSM and simulation with Modelsim
  - You can find all the files about this exercise in the dedicated folder on the Team of the course
    - File > Electronics Systems module > Crocetti > Exercises > 2.4
  - Try to simulate on your own
  - However, I also included two .do files to automate the waveform and the simulation
    - wave.do and sim.do
    - Refer to README.txt file
    - Look at the wave.do file, if you are curious about how to display labels for the current state





Thank you for your attention

Luca Crocetti  
(luca.crocetti@unipi.it)