



Electronics Systems (938II)

Lecture 3.2

Semiconductor Memories – ROM and PROM

ROM

- **ROM = Read-Only Memory**

- However, **this gives information only on the supported operation(s)**

- I.e., read-only (not write)

- It **does not give information on the access mode** (random or sequential)

- Typically, **this kind of memories supports random access**

- I.e., any arbitrary address can be accessed immediately


- **So, it is also a RAM**

- Please, do not confuse with the computer memory typically called RAM, which is a RAM (from the perspective of access mode), but it is also a RWM (Read-Write Memory)

} ROM typically implemented as RAM.

ROM – Architecture

 - Brief reminder of the structure of semiconductor memories
 - WL_i = Word Line
 - BL_j = Bit Line




ROM – Architecture

- Brief reminder of the structure of semiconductor memories


- WL_i = Word Line
- BL_j = Bit Line

- In case of ROM, the memory cell can be

- 1 n-MOS transistor

 

- Empty

 


ROM – Architecture

- Memory cell – n-MOS transistor

- WL_i = Word Line
- BL_j = Bit Line


- n-MOS

- D = Drain
- G = Gate
- S = Source

 

ROM – Architecture

 - Memory cell – n-MOS transistor
 - WL_i = Word Line
 - BL_j = Bit Line
- n-MOS
 - D = Drain
 - G = Gate
 - S = Source
- To complete the architecture ...



ROM – Architecture

- Memory cell – n-MOS transistor


- WL_i = Word Line
- BL_j = Bit Line

- n-MOS

- D = Drain
- G = Gate
- S = Source


- R = Resistor

 - Pull-up resistor: connect BL_j to V_{CC} = high logic level (1)




ROM – Architecture

 - Memory cell – n-MOS transistor
 - Principle of operation



ROM – Architecture

 - Memory cell – n-MOS transistor
 - Principle of operation
 - $WL_i = 0$
 - n-MOS = OFF (open circuit)
 - $BL_j = 1$ (because of pull-up resistor)



ROM – Architecture

- Memory cell – n-MOS transistor


- Principle of operation

- $WL_i = 0$

- n-MOS = OFF (open circuit)
 - BL_j = 1 (because of pull-up resistor)

- $WL_i = 1$

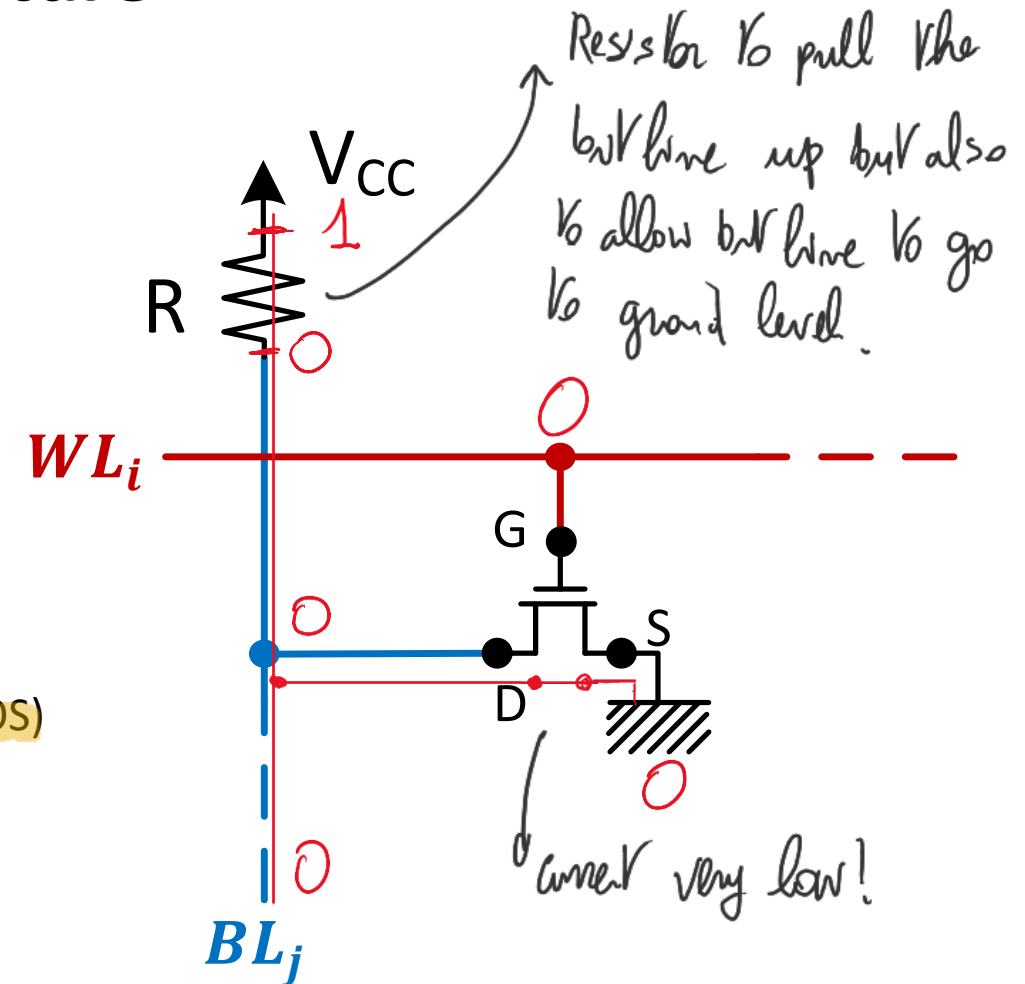- n-MOS = ON (short circuit)
 - BL_j = 0 (ground connection through the n-MOS)




ROM – Architecture

- Memory cell – Empty

- Principle of operation

 - $WL_i = 0$
 - $BL_j = 1$ (because of pull-up resistor)
 - $WL_i = 1$
 - $BL_j = 1$ (because of pull-up resistor)



ROM – Architecture

- Memory cell – Summary
 - Principle of operation

Memory cell	Word Line (WL_i)	Bit Line (BL_j)
With n-MOS	0 (disabled)	1
	1 (enabled)	0
Empty	0 (disabled)	1
	1 (enabled)	1


On bitline you have the output of the bit block.

ROM – Architecture

- Integrating the row and column decoders to complete the architecture

ROM – Architecture

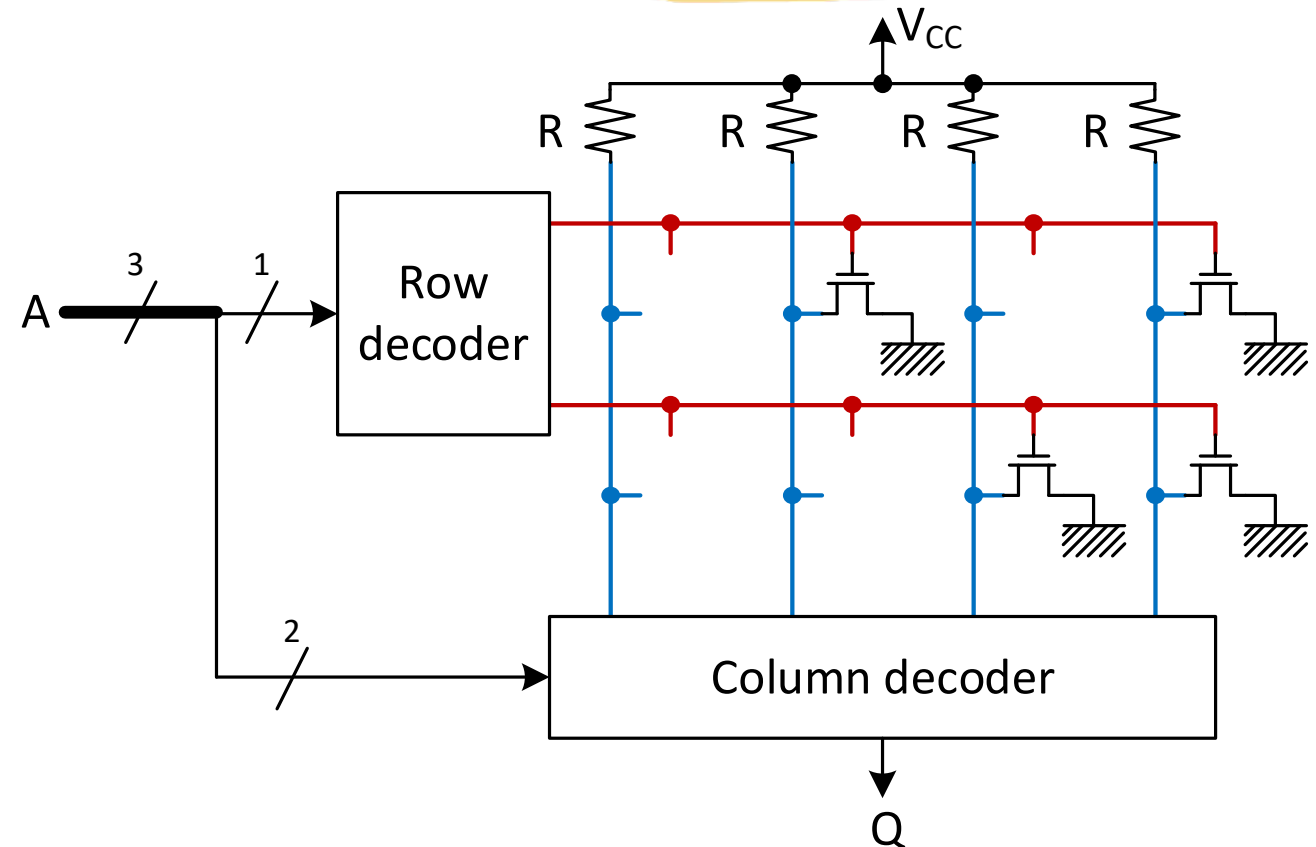- Integrating the row and column decoders to complete the architecture
 - Example on a 2x4 ROM
 - A = Address (3-bit)
 - Q = single-bit output




ROM – Architecture

- Integrating the row and column decoders to complete the architecture

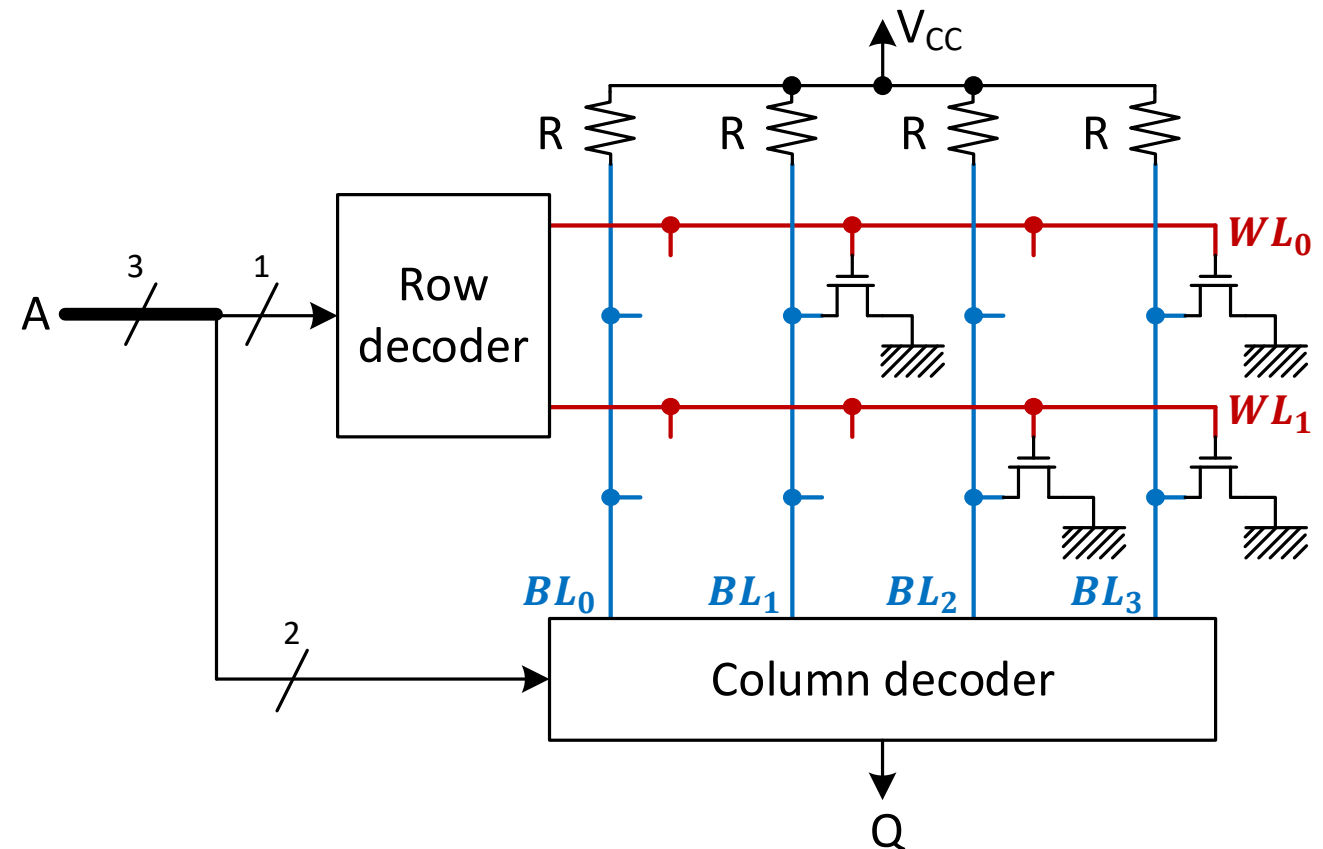- Example on a 2x4 ROM

- A = Address (3-bit)
 - Q = single-bit output
- Assume cell (x,y)
 - WL_x
 - BL_y



ROM – Architecture

- Integrating the row and column decoders to complete the architecture


- Example on a 2x4 ROM

- A = Address (3-bit)
- Q = single-bit output

- Assume cell (x,y)

- WL_x
- BL_y

- Assume to read cell (1,1)

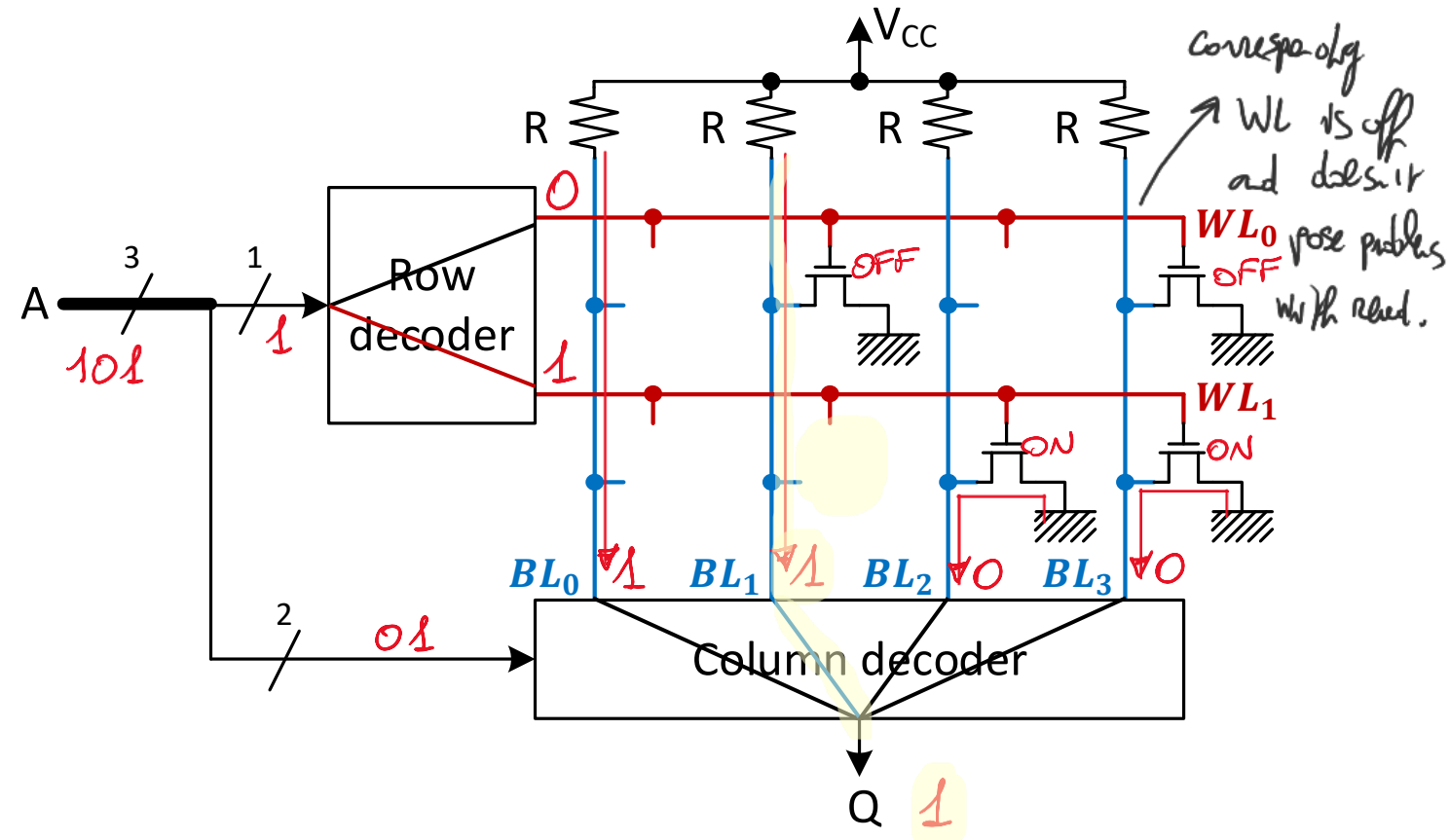

ROM – Architecture

- Integrating the row and column decoders to complete the architecture


- Example on a 2x4 ROM

- A = Address (3-bit)
- Q = single-bit output

- Assume **cell (x,y)**

- WL_x
- BL_y

- Assume to read **cell (0,1)**

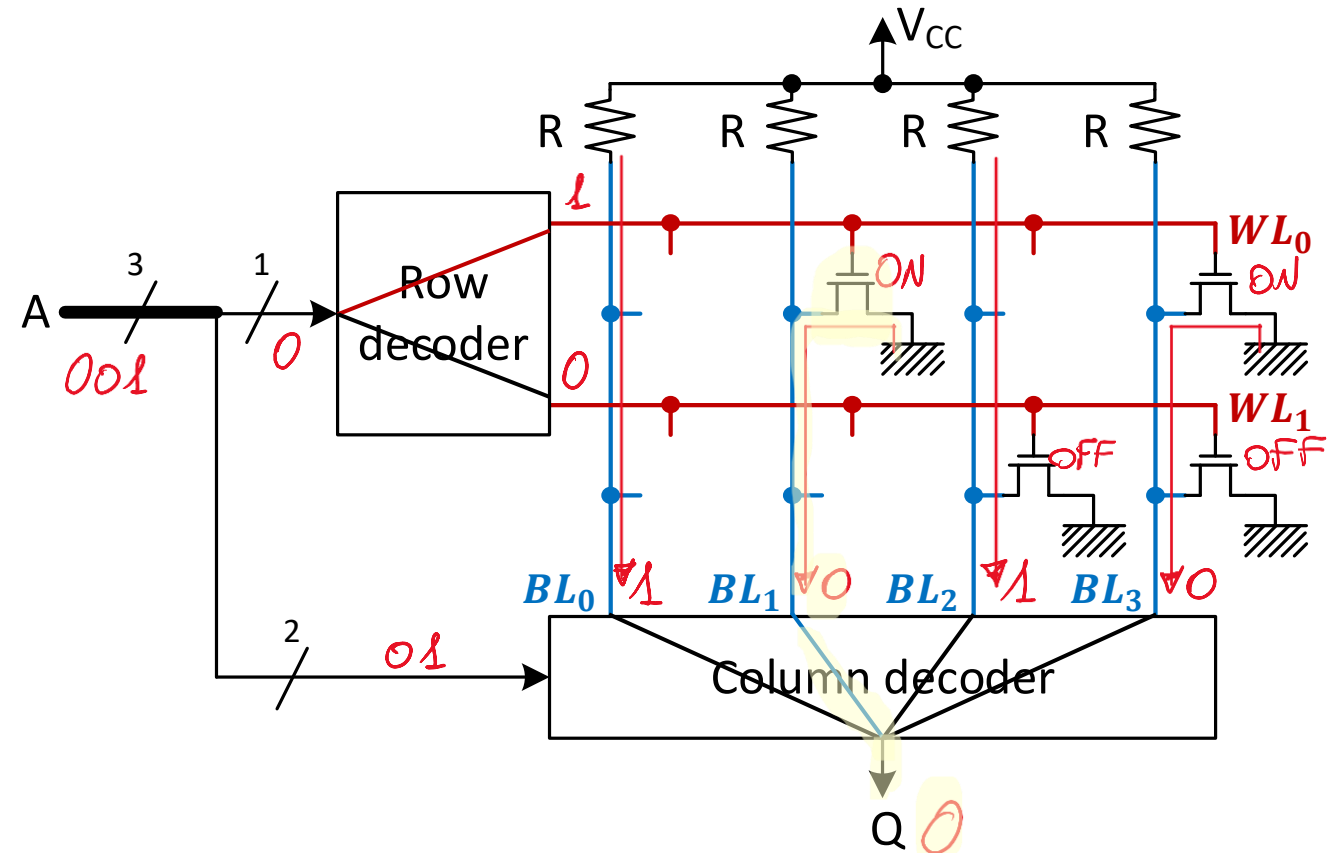

ROM – Architecture

- Integrating the row and column decoders to complete the architecture


- Example on a 2x4 ROM

- A = Address (3-bit)
- Q = single-bit output

- Assume **cell (x,y)**

- WL_x
- BL_y

- Assume to read **cell (1,3)**

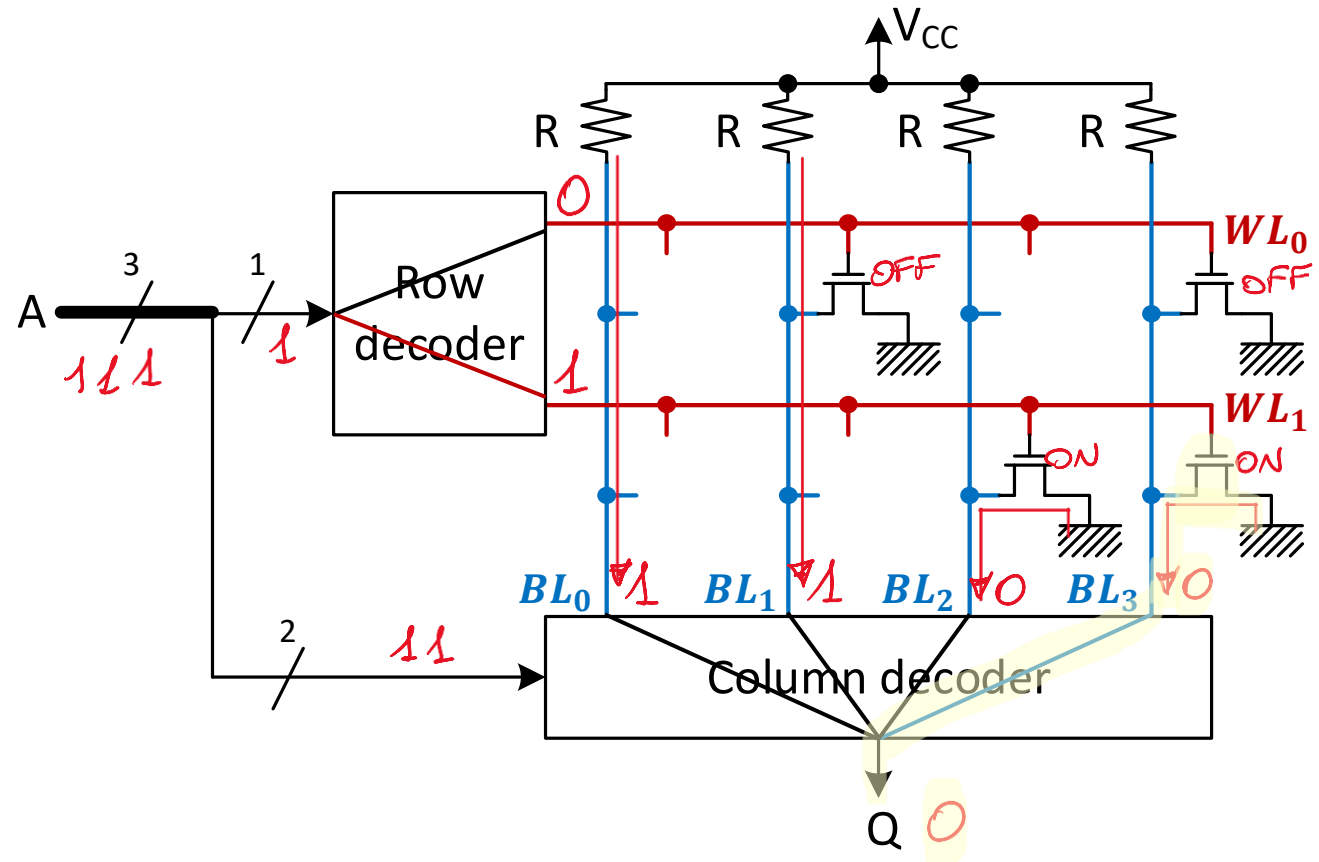

ROM – Architecture

- Integrating the row and column decoders to complete the architecture


- Example on a 2x4 ROM

- A = Address (3-bit)
- Q = single-bit output

- Assume **cell (x,y)**

- WL_x
- BL_y

- Assume to read **cell (0,3)**

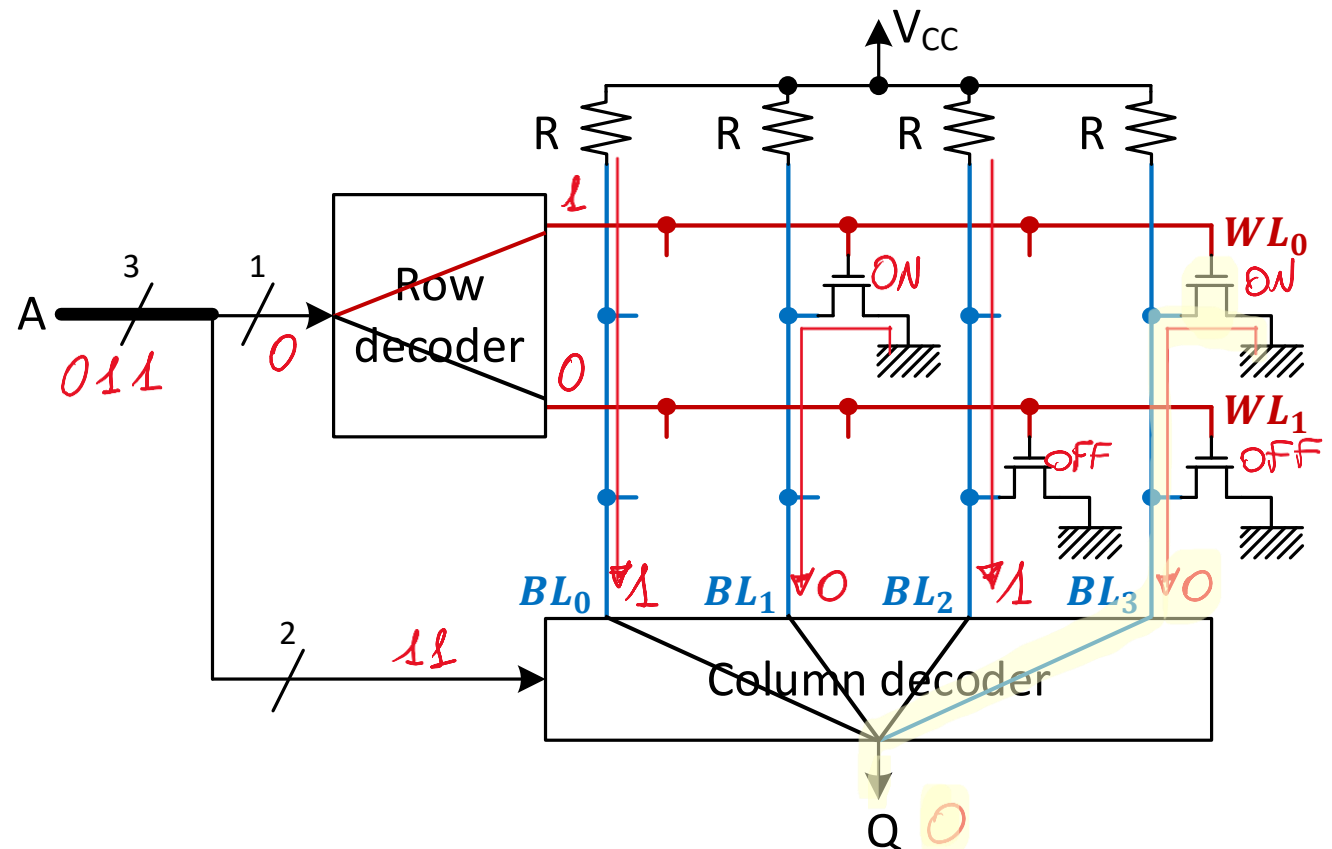

ROM – Architecture



- So, when reading (i.e. enabling corresponding word line and bit line) a memory cell
 - With (n-MOS) transistor → Output = 0
 - Empty (without transistor) → Output = 1

*This is for active high logic
↓ Depends on decoding logic*
- However, also solutions with active-low decoding logic (for column decoder) exist

↳ out = opposite of what you have on the bitline.

ROM – Architecture

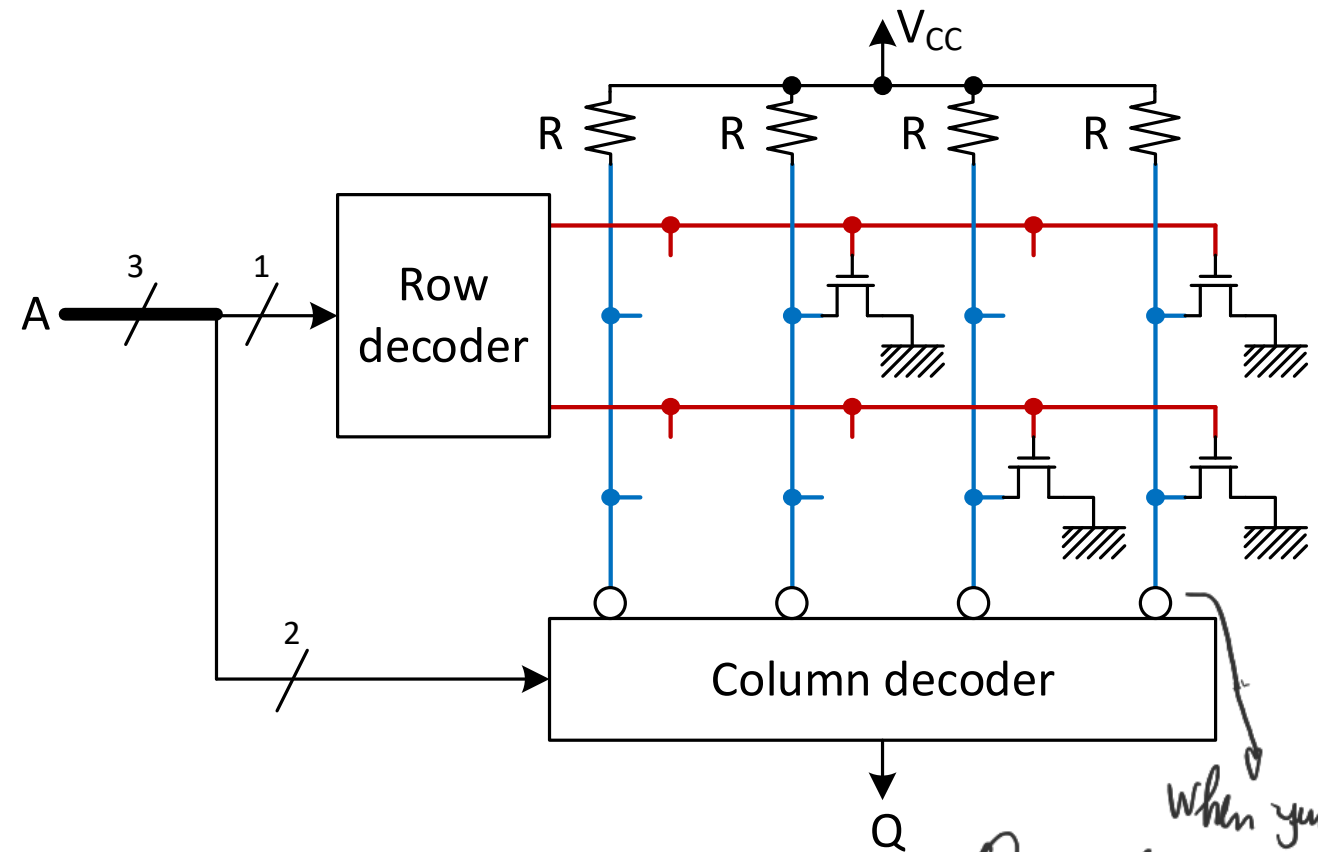 
- Active-low decoding logic (column decoder)
 - Example on a 2x4 ROM



ROM – Architecture

- Active-low decoding logic (column decoder)
 - Example on a 2x4 ROM

- Assume to read **cell (0,3)**

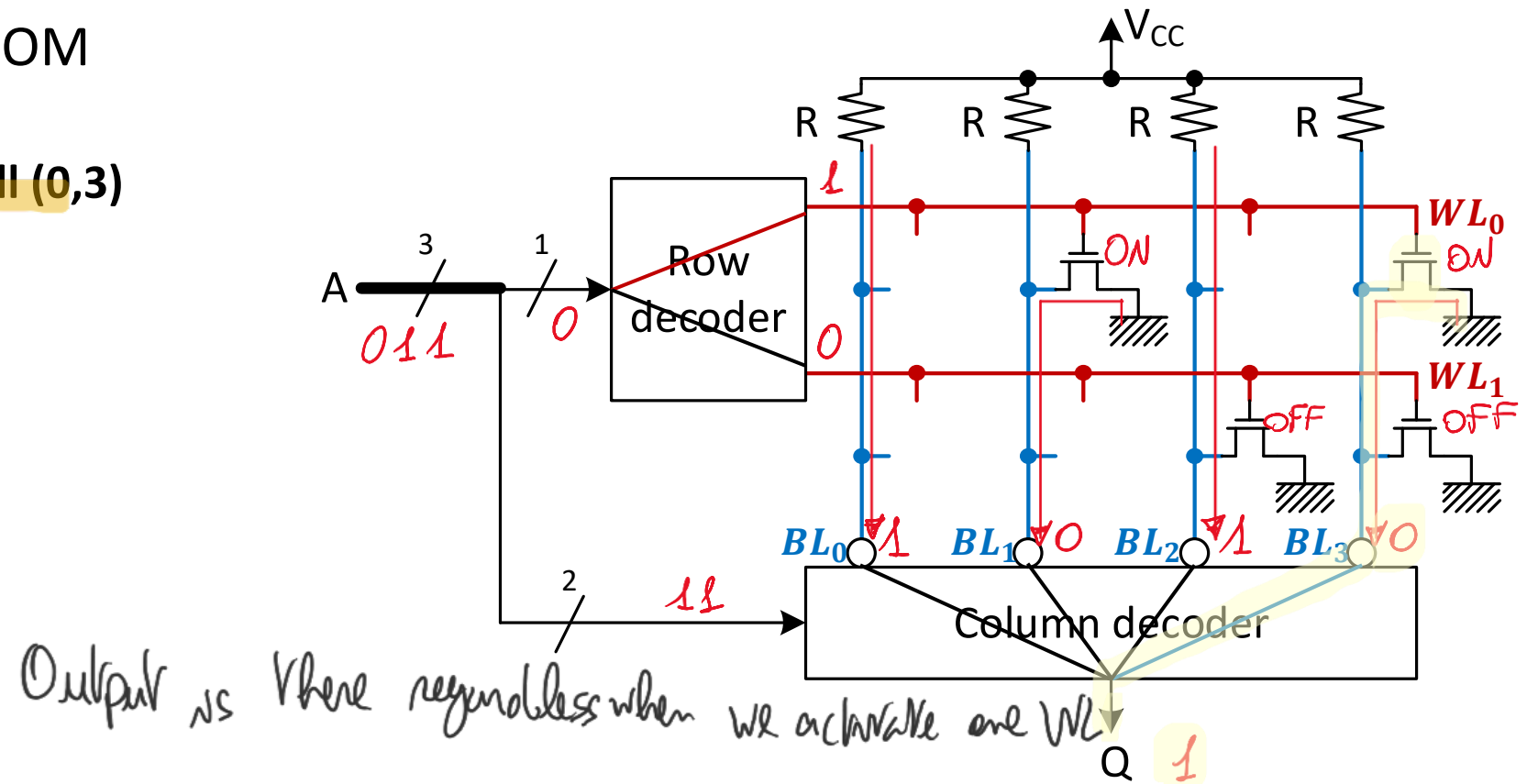

ROM – Architecture

- When reading a memory cell when column decoder is active-low

- With (n-MOS) transistor → Output = 1
- Empty (without transistor) → Output = 0

Why? To see all the possibilities.

- The opposite of the previous case

Value stored depends about the decoding logic. In general Active low is more used.

ROM – Architecture

- Content of memory cells
 - The output (bit) corresponds to the content of memory cells, since that is what is obtained by reading that cell

Memory cell	Bit Line (BL_j)	Output (bit) = Content	
		Active-high decoding logic	Active-low decoding logic
With n-MOS	0	0	1
Empty	1	1	0

ROM – Remarks and applications

- The one shown is called also **mask-ROM**
 - Remember about the photolithographic masks employed in the semiconductor manufacturing process
 - Each memory content corresponds to a different layout (of transistors), or, in other words, to a different integrated circuit
 - Thus, to a different mask to realize that layout (or circuit)

ROM – Remarks and applications

- Photolithographic masks have high costs *↑ low cost!*
 - Only for applications that require high volumes of ROM
- Memory content cannot be modified
 - The modification of just one bit (due to updates or bugs) means wasting the entire chip (and all other chips with the same content)
 - Only for solid applications for which you are largely sure about the content of the memory

PROM

- In the course of technological progress, mask-ROM has evolved into **Programmable ROM (PROM)** *[Don't say write, say program the memory]*
 - ↳ Programming is destructive (this is true for programmable mems)
- Still a ROM, Read-Only Memory
- But whose content is defined after the manufacture (of the integrated circuit)
 - Not during the manufacture like the mask-ROM
- This allowed for a reduction in production costs because ...
 - For mask-ROMs: different memory content → different integrated circuit → different production line (masks, ...)
 - For PROM: always the same integrated circuit → the same production line

PROM


- So, after production the PROM must be “written” to define its content
 - This operation is called Programming
 - From here the name
 - Just one time
 - OTP = One Time Programmable *old name*

PROM

- So, after production the PROM must be “written” to define its content
 - This operation is called Programming
 - From here the name
 - Just one time
 - OTP = One Time Programmable
- For this purpose, **each memory cell contains a transistor + a fuse**
 - The **fuse** is an electronic component that ...
 - ... by **default, is a connection** (a short circuit)
 - ... when **subjected to a very strong current, it breaks down, breaking the connection** (it becomes an **open circuit**)


PROM – Architecture

- Memory cell

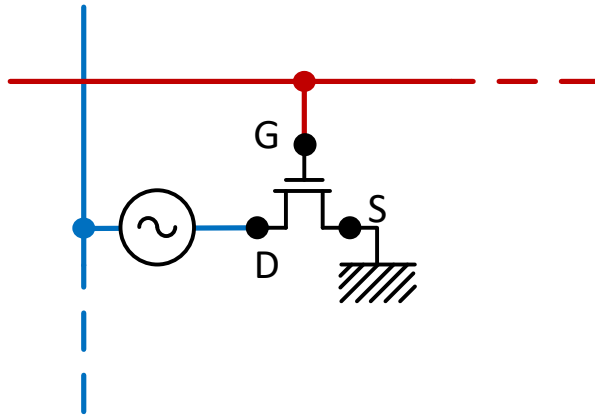


PROM – Architecture

 - Memory cell
 - Transistor (n-MOS) *in all memory cells*





PROM – Architecture

 - Memory cell
 - Transistor (n-MOS)
 - Fuse




PROM – Architecture

  - Memory cell
 - Transistor (n-MOS)
 - Fuse



PROM – Architecture

 - Memory cell
 - Transistor (n-MOS)
 - Fuse




PROM – Principle of operation

- Thus, programming means selecting which fuses to break (by injecting a high current)
 - Programmed fuse = broken fuse = open circuit
 - Unprogrammed fuse = default-state fuse = short circuit

PROM – Principle of operation

 - For this purpose, high voltage pulses ($V_{PP} = 10/30\text{ V}$) must be applied to
 - Gate terminal of n-MOS = Word Line
 - Drain terminal of n-MOS = Bit Line
 - n-MOS is in “high conduction” region = very high current




PROM – Principle of operation

- By selecting (only) the corresponding Word Line and Bit Line, each memory cell can be programmed (or not) without the risk of accidentally programming cells that should do not
 - A dedicated interface is required
- After programming, the PROM works exactly like the mask-ROM
 - Not programmed cell = cell with transistor → 0 on BL → 0/1 on output (Q)
 - Programmed cell \cong empty cell → 1 on BL → 1/0 on output (Q)


PROM – Principle of operation

- Example
 - Before programming

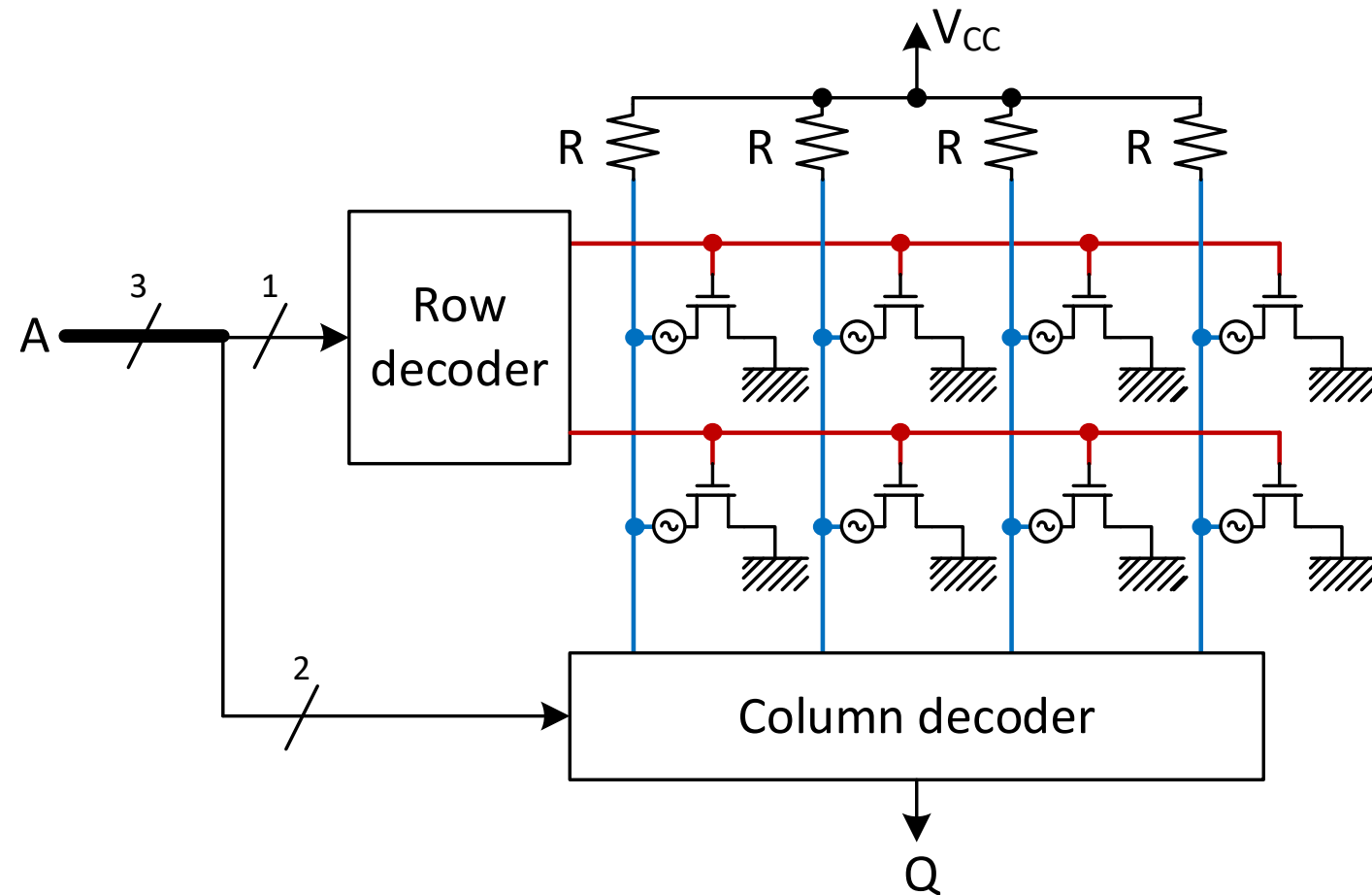


PROM – Principle of operation

- Example
 - After programming

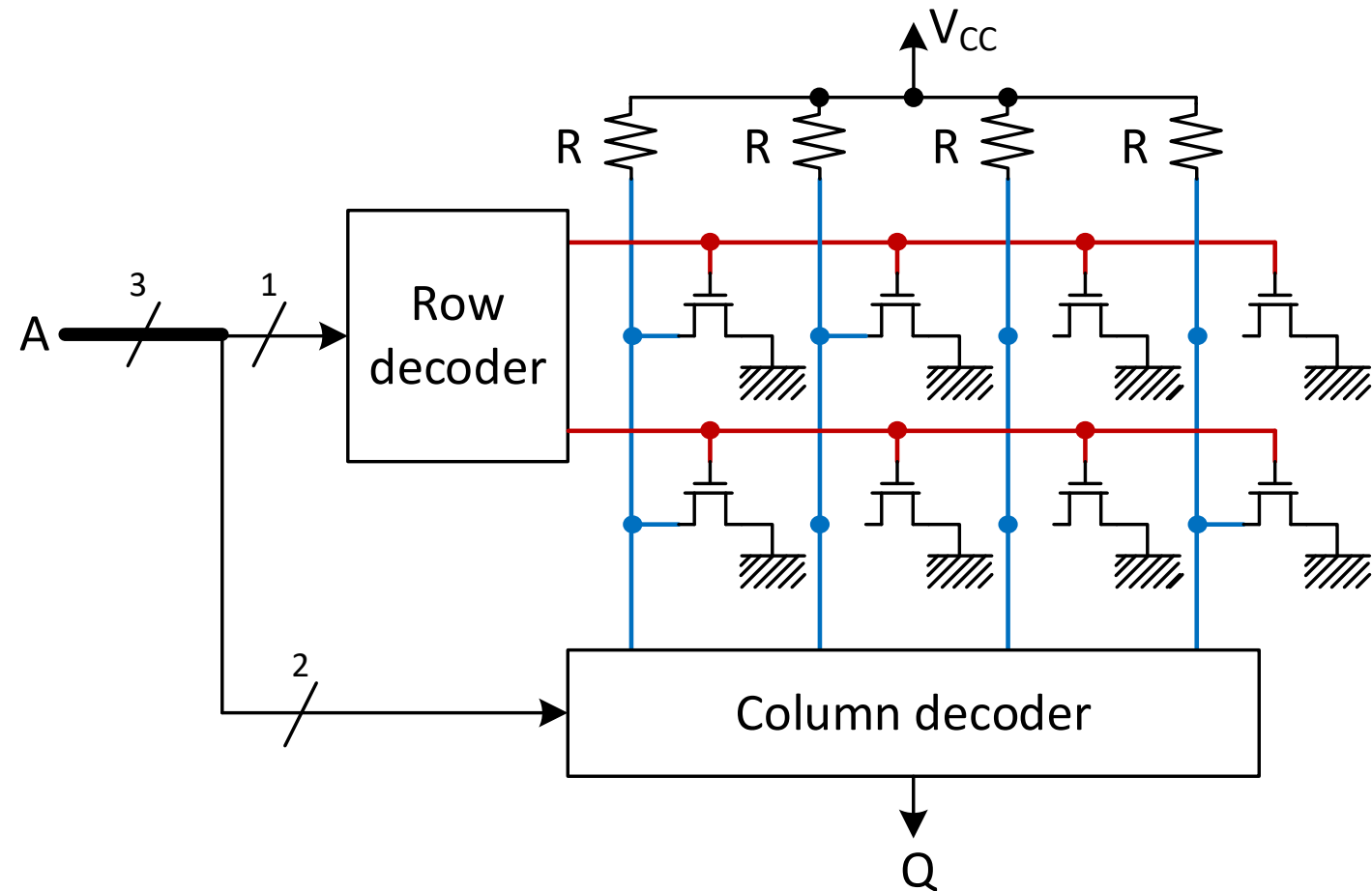


PROM – Principle of operation

- Example
 - Reading cell (0,2)

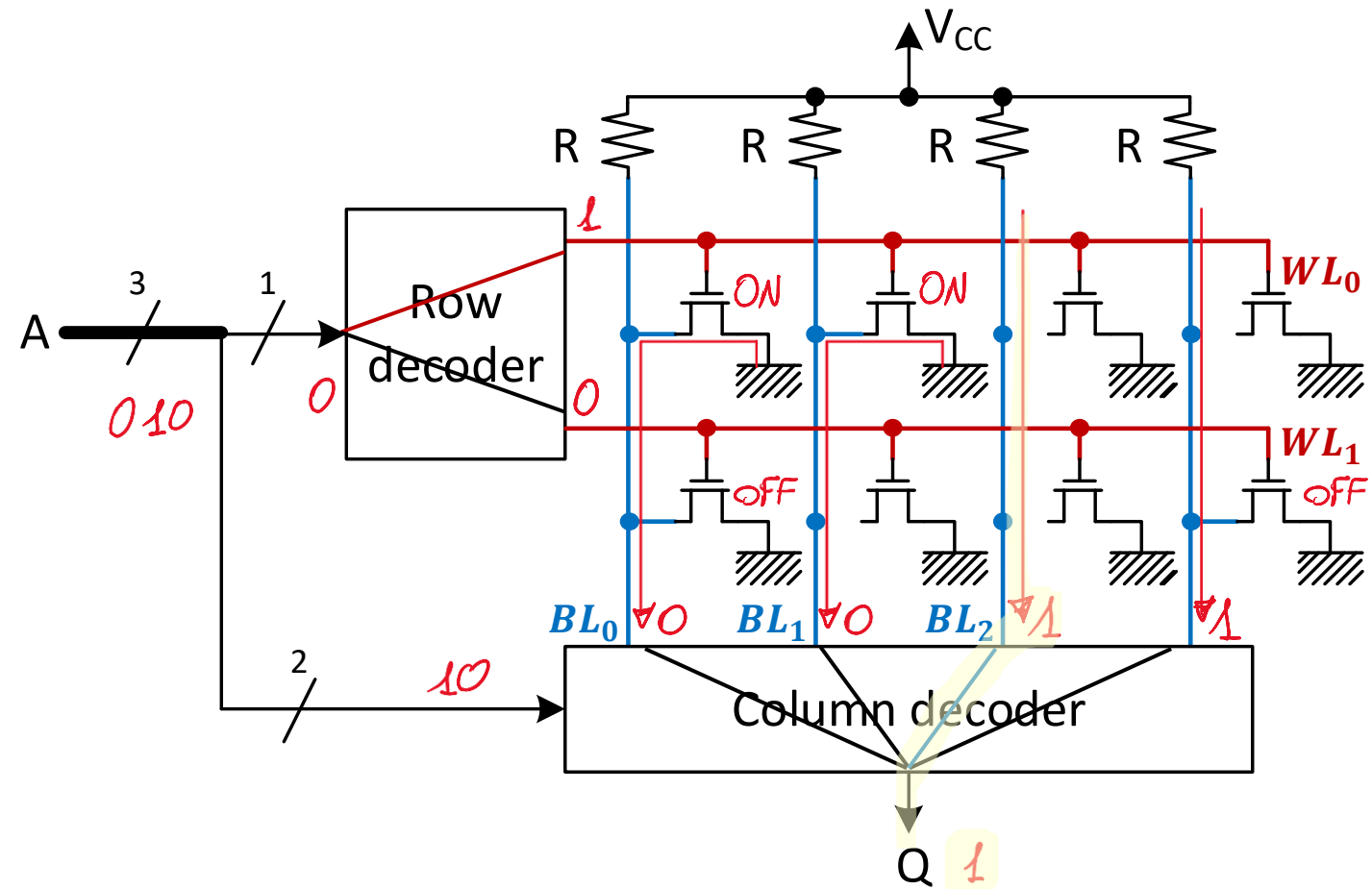

PROM – Remarks and applications

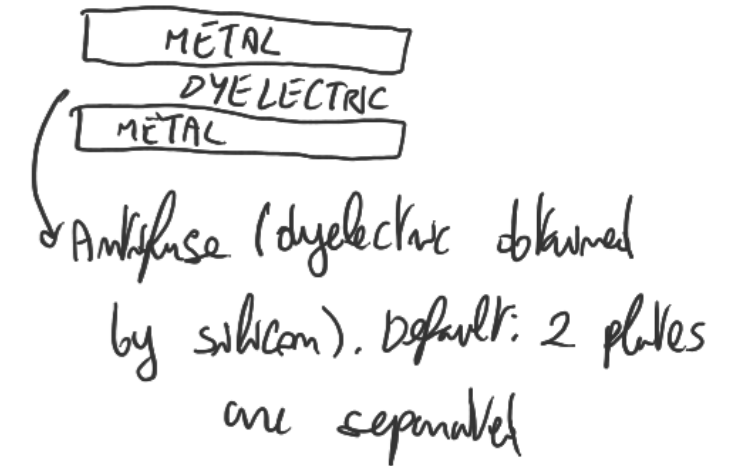- **Anti-fuses** can be used instead of fuses
 - Opposite of fuse
 - Default (not programmed) = open circuit
 - Programmed (with high current flow) = short circuit
- Early PROMs had reliability problems
 - Incompletely vaporized fuses
 - Floating shrapnel inside the IC package
- Target applications
 - The same as mask-ROMs





Thank you for your attention

Luca Crocetti
(luca.crocetti@unipi.it)